

Conducted Susceptibility CS101




Raymond K. Adams
Fischer Custom Communications, Inc.
20603 Earl Street
Torrance, CA 90503
(310)303-3300
radams@fischercc.com


CS101

- Applicability
 - DC and AC Input Power Leads
 - Does NOT include RETURNS or Output Power Leads
- Frequency Ranges
 - DC Power: 30 Hz to 150 kHz
 - 60Hz Power: 120 Hz to 150 kHz
 - 400Hz Power: 800 Hz to 150 kHz

2

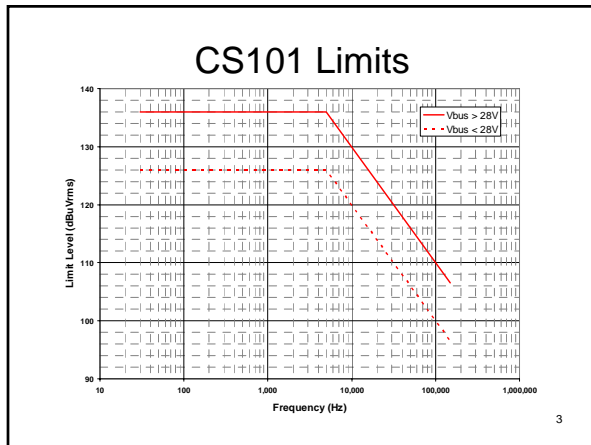

3

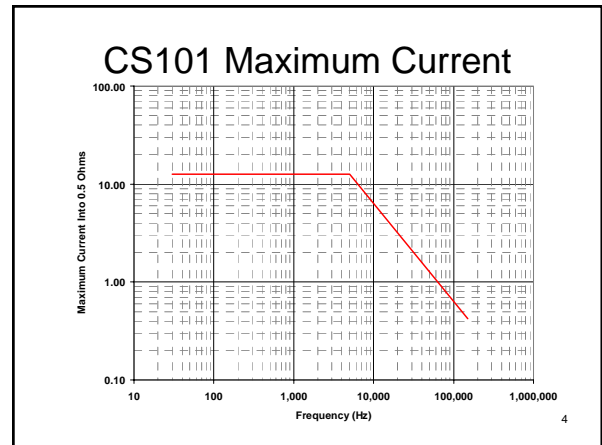


4

Basis For CS101 Limits

- Similar to CE102
- Based on Review of Power Quality Standards
- Emphasis on MIL-STD-704 Spectral Content Curves
- Voltage Amplitude Is Approximately 6 dB above typical power quality limits and is somewhat generalized to avoid complex curves
- Difference Between CE102 and CS101 of 26 dB SHOULD NOT be viewed as MARGIN
- CE102 Limit Set Such That Ripple Voltages Do Not Exceed That Allowed By Power Quality Standards For Multiple Unit Contributions
- Power Quality Standard is ONLY VALID Basis of Comparison
- Tailoring Limit Is Allowable But Primary Consideration Should Be To Closely Follow A Particular Power Quality Standard


5

Comparison To MIL-STD-704 28Vdc or Less

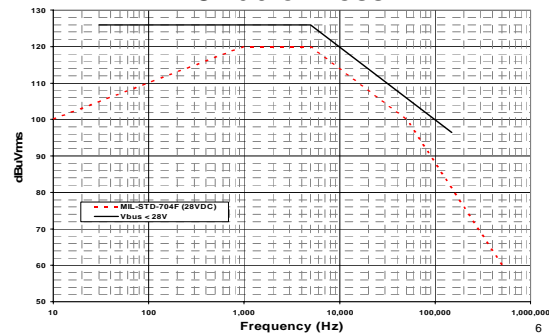

6

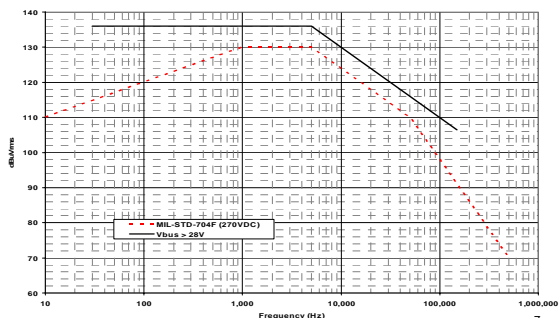Comparison To MIL-STD-704 Greater Than 28Vdc



7

CS101 Test Procedure

- Calibrate Test Setup Across 0.5 Ohm Resistor
- Configure Test Setup Properly For Power Type (DC, AC Single Phase, Three Phase AC)
- Power Up EUT and Allow Time To Stabilize
- Inject The Required Interference Voltage Level Per The Approved EMC Test Procedure Into The EUT
- If Unable To Inject The Required Voltage STOP At The Predefined Current or Power Limit Into 0.5 Ohm Load.


8

CS101 Test Procedure

- Use Table III of Paragraph 4.3.10.4.1 as a guideline for Maximum Scan Rates or Maximum Stepped Frequencies
- Observe Minimum Dwell Times And Adjust As Necessary
- Monitor The EUT For Susceptibility
- Threshold The EUT As Required
- Repeat For All Required Voltage Lines or EUT Operational Modes
- Document The Test Results


9

CS101 Calibration Setup

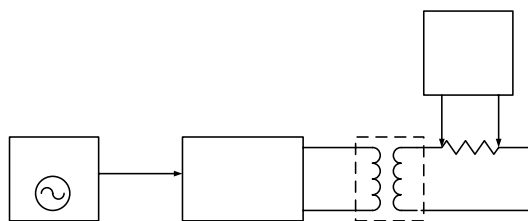


10

DC or Single Phase AC

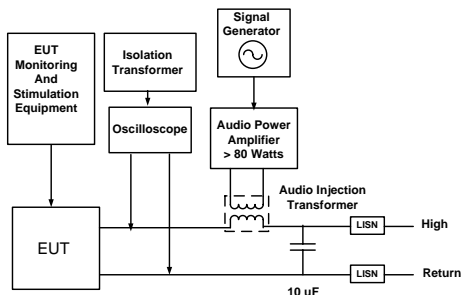

11

Three Phase AC Ungrounded

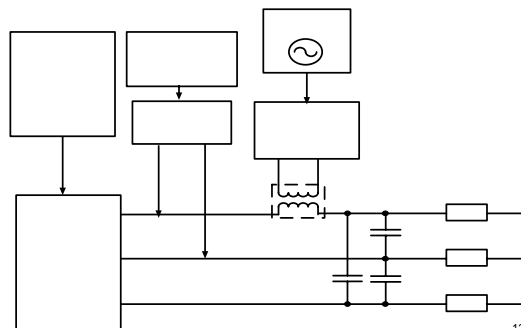


12

Three Phase Ungrounded (Three Wire)

Coupling Transformer in Line	Voltage Measurement From
Phase A	Phase A to Phase B
Phase B	Phase B to Phase C
Phase C	Phase C to Phase A

13

Three Phase AC WYE

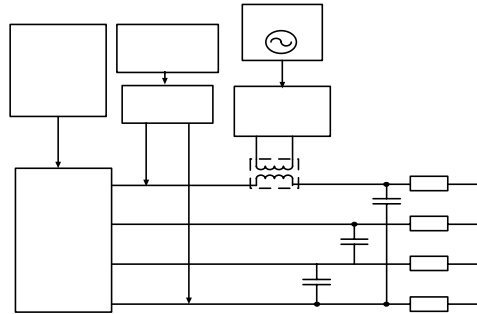

14

Three Phase Wye (Four Wire)

Coupling Transformer in Line	Voltage Measurement From
Phase A	Phase A to NEUTRAL
Phase B	Phase B to NEUTRAL
Phase C	Phase C to NEUTRAL

15

Basis For CS101 Scan Rates

- Assumed Maximum Response Time of 3 Seconds Considered Appropriate For Large Percentage of Possible Cases
- Typical "Q" Values of 10 or less for Frequencies Below 1 MHz
 - $Q = f_0/BW$
- Analog Scan Rate $0.0333 f_0 / \text{Sec}$
- Stepped Scans $0.05 f_0$

16

Adjustments To Scan Rates

- The Time An EUT Is In Susceptible State May Be Limited, THEREFORE Scan Rates Must Be Adjusted.
- Mechanical Outputs May Require More Time To Respond Than Electronic Outputs.
- Analog Scan Rates May Be Inappropriate In Some Cases And Stepped Scans With Long Dwell Times May Be Required.
- Using Stepped Guidelines, 176 Frequency Steps Are Required For The Entire CS101 Range

17

Threshold of Susceptibility

- When Susceptibility Is Detected Reduce Interference Signal Until EUT Recovers
- Reduce Interference By an Additional 6 dB
- Gradually Increase Interference Until Susceptibility Reoccurs. The Resulting Level Is The Threshold Of Susceptibility
- Record This Level, Frequency Range Of Occurrence, Frequency And Level Of Greatest Susceptibility And Other Test Parameters As Applicable.

18

CS101 Analog Scan Rates

Frequency Range	Maximum Scan Rate	Actual Scan Time
30 Hz – 100 Hz	1 Hz / Sec	1.2 Minutes
100 Hz – 1 kHz	3.33 Hz / Sec	4.5 Minutes
1 kHz – 10 kHz	33.3 Hz / Sec	4.5 Minutes
10 kHz – 100 kHz	333 Hz / Sec	4.5 Minutes
100 kHz – 150 kHz	3.33 kHz / Sec	0.3 Minutes
TOTAL SCAN TIME		~ 15 Minutes

19

Comments About Injection Transformer Use

- May Be Required If Power Return Not Connected To Shielded Room Ground
 - Electrically “Floats” Oscilloscope
 - Creates Potential Shock Hazard!
- Differential Voltage Measurement Preferable
 - Eliminates Floating Oscilloscope
 - Eliminates Potential Shock Hazard
- Digital Oscilloscope Using Two Channels and Waveform Math
- Differential Voltage Probes


20

Comments About AC Power

- Monitoring Injected Voltage Can Be Difficult on AC Lines
 - AC Power Frequency Voltages Much Larger Than CS101 Injected Signal
 - Typically, 25 to 65 dB!
 - Limited Dynamic Range of Oscilloscopes
 - Aliasing of Digital Oscilloscopes
 - Difficult, if not impossible to SIMULTANEOUSLY display large amplitude low frequency signal and low amplitude high frequency signal with accuracy!


21

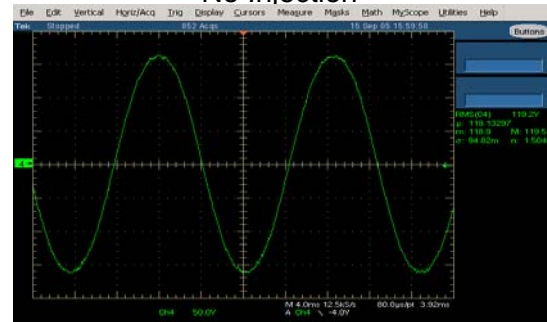120VAC, 60 Hz EUT Monitoring No Injection




22

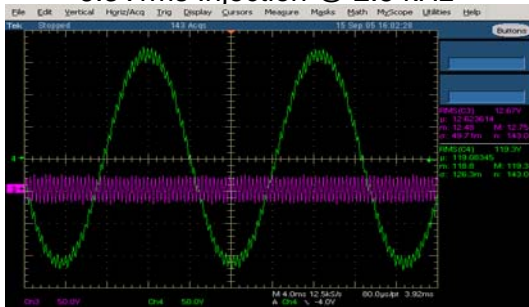120VAC, 60 Hz EUT Monitoring 6.3Vrms Injection @ 2.5 kHz




23

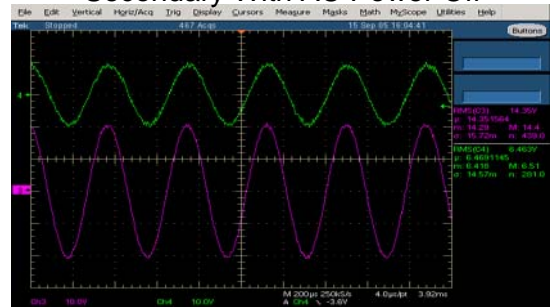Transformer Primary and Secondary With AC Power Off



24

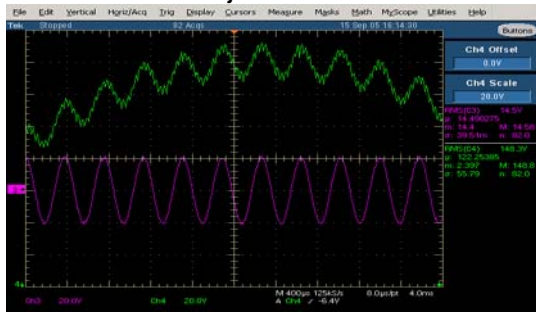ZOOM IN: 120VAC, 60 Hz EUT Monitoring 6.3Vrms Injection @ 2.5 kHz




25

Comments About AC Power

- AC Line Voltage on Transformer Primary Induces Voltage on Transformer Secondary
 - High Current Loads Produce Larger Voltages
 - 400Hz Produces A Larger Voltage Than 60Hz
 - Significant Line Voltage Component Induced into Power Amplifier Output
 - Can Cause Problems or Damage Amplifier
- Impact on Power Amplifier Can Be Minimized
 - Two Identical Injection Transformers
 - Dummy Load
 - Same Current Draw
 - Same Power Factor


26

AC Line Voltage Into Amplifier

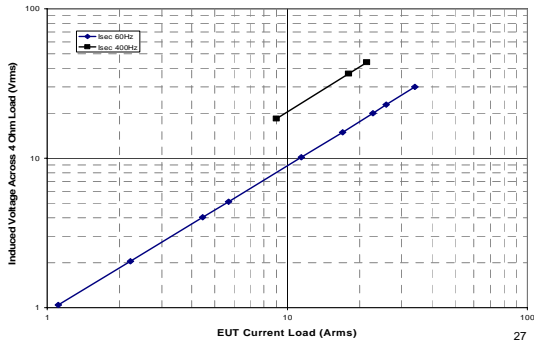

27

AC Line Power Into Amplifier

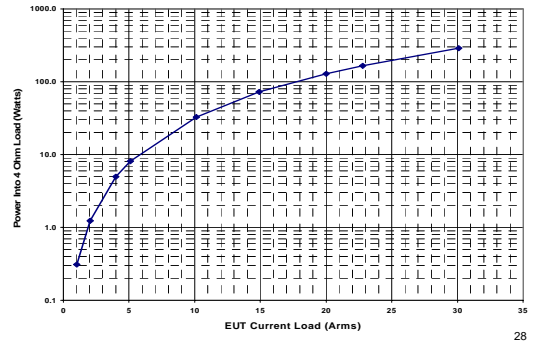

28

Comments on AC Power (Continued)

- Impact on Power Amplifier Can Be Minimized (Continued)
 - The Secondary Side of Transformers Have Equal Loads
 - The Primary Sides are wired such that the loads are 180 Degrees out of phase
 - Thus “nulling” the AC Line Frequency component injected into the power amplifier output

29

Comments on AC Power (Continued)

- Practical Limitations
 - Power Factor difference between EUT and Dummy Load
 - Phase Difference Impacts Cancellation
 - Difference in Injection Transformer
 - Voltage Amplitudes of Transformer Primaries


30

Phase and Amplitude Imbalance

- The Imbalance Between The Amplitude And Phase Is Important
 - Phase Must be Within +/- 10 Degrees and Amplitude Within 6 dB for Rejection Better Than 6 dB!
 - See Graph


31

Phase & Amplitude Imbalance

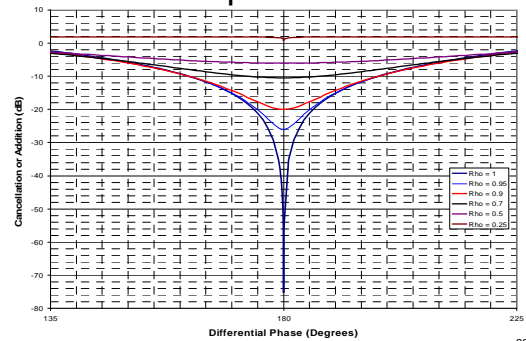


32

Setup Without Floating O'Scope

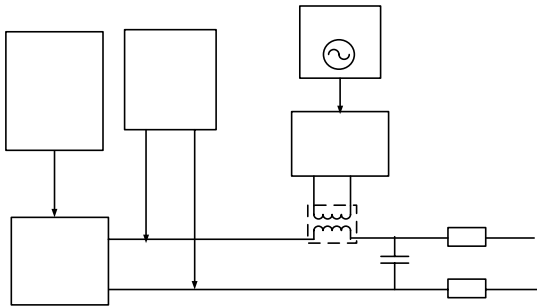

33

Setup Without Floating O'Scope

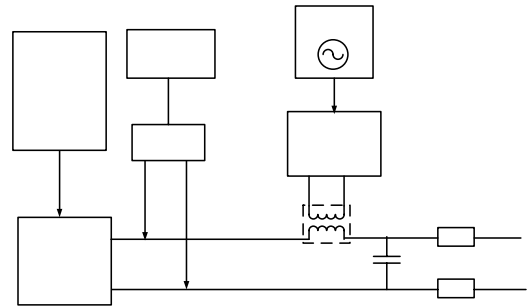


34

Comments About 10 uF Capacitors

- The 10uF capacitor is meant to “control” the injected signal loop.
 - The 10uF is not ideal at low frequencies
 - $X_c \sim 530$ ohms at 30 Hz
 - Suggest using larger capacitor (~10k uF) with appropriate voltage ratings to better control the injected signal loop

35

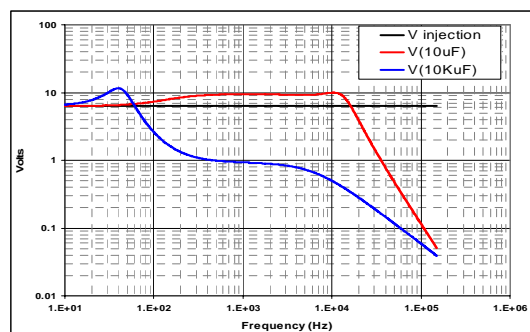Replace 10uF Capacitor With 10kuF Capacitor



36

EUT
Monitoring
And
Stimulation
Equipment

Oscilloscope


Waveform Math
Ch A + (Ch B)Inverted

Ch A

Ch B

Generator

Audio Power



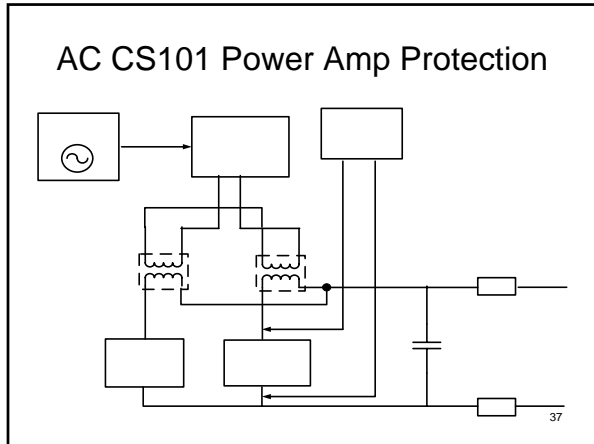


Signal
Generator

Audio Power
Amplifier
> 80 Watts

Voltage
Monitoring
Device*

*Oscilloscope
OR
Spectrum Analyzer

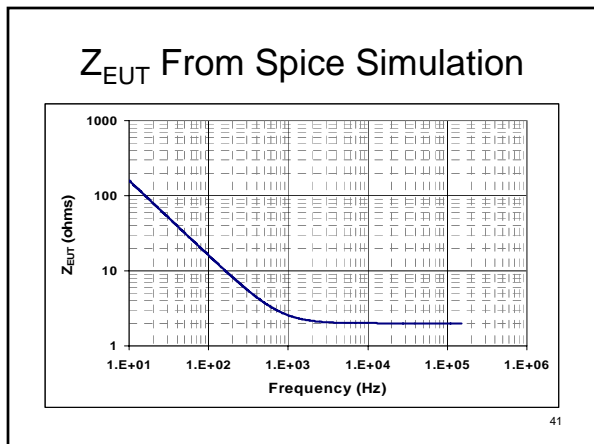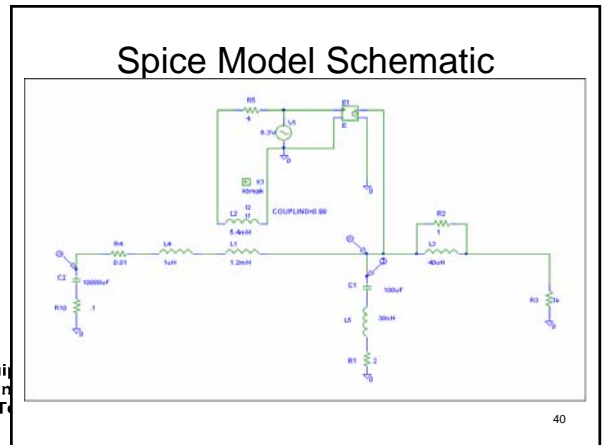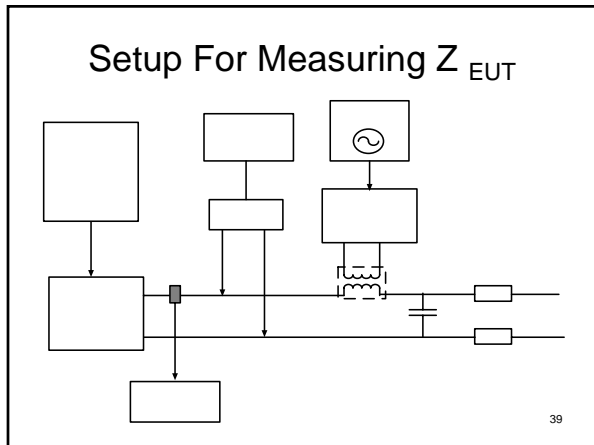

EUT
Monitoring
And
Stimulation
Equipment

Spectrum
Analyzer
(Voltage)

- ### Modeling The CS101 Test Setup
- Evaluate EMI Filter Design
 - Find Problems Early
 - Correct Sizing Of Damping Resistor Wattage
 - Compare To Current/Wattage Limits
 - Can Help With Troubleshooting Out-Of-Specification Conditions
 - Test Data Should Trend Spice Simulation
 - Injected Voltage
 - Injected Current
 - Impedance

Signal
Generator

Differentia
Voltage
Probe

Audio Power
Amplifier

EUT Monitoring Considerations

- If EUT Current Draw Varies Significantly
 - Test At Low EUT Current
 - Test At Nominal Current
 - Test At High EUT Current
- Non Air Core Inductors Will Lose Inductance With Increased Current
 - Design With This In Mind
 - Can Be Modeled In Spice With BH Curves If Available
- Bus Voltages
 - Always Set Voltage At EUT Under Load
 - Nominal, Minimum and Maximum
 - Injected Ripple When Imposed On Minimum Voltage Can Be Problematic If EUT Has Linear Regulator.

43

Summary

- Conducted Susceptibility Test Limits Are Based Upon Power Quality Specifications Not CE102 Levels.
 - Tailoring Is Allowable With This In Mind
- Scan Rates Are Based Upon Unit Q of 10 And Assumed 3 Second EUT Response Time
 - Scan Rates Should Be Adjusted If Necessary
- If Voltage Level Can Not Be Met Use Power Limit Curve Into 0.5 Ohms
- 10uF Capacitor Should Be Increased To "Control" Injected Signal Loop.
- AC CS101 Testing Starts At 2nd Harmonic
- Monitoring The Injected Voltage on AC Power Lines Is Difficult With An Oscilloscope.
 - Recommend Using A Spectrum Analyzer or EMI Receiver With Properly Rated Probe
- Specific Injection And Monitoring Configurations Are Outlined For Single Phase, Three Phase Ungrounded, And Three Phase Wye

44

Summary (Continued)

- AC High Current EUT Can Induce Significant Voltages Into The Power Amplifier Via The Injection Transformer And Damage Power Amplifier
- Power Amplifier Can Be Protected With Two Transformers
 - Primaries Phased To Cancel Power Line Frequency
 - Secondaries Are Tied To EUT and Dummy Load of Same Current /Power Factor
- Modeling The Input EMI Filter With Spice Is A Valuable Tool
 - Can Find Problems Early
 - Check Input Damping Resistor Power Rating
 - Can Let You Know What To Expect BEFORE The Test
 - Can Be Used In Conjunction With Test Data To Check Schematic To "As Built" For Errors
- Account For Heavy Current Loads When Sizing Non Air Core Inductors
 - Test Multiple Current Levels
- Always Set EUT Voltage At EUT Under Load
 - Account For Voltage Drops
 - Know Whether To Test At Nominal, Minimum or Maximum Voltage(s)
 - Be Wary Of EUT's With Linear Regulation

45