

Energy Efficient Multi-Gb/s I/O: Circuit and System Design Techniques

April 22, 2011

WMED-2011

Bryan Casper, Intel Circuit Research Labs

Agenda





Introduction



- Impact of process scaling
- Active power optimization
 - System
 - Circuit
- Power management
- Low power silver bullets
- Putting it all together

High-End Server

  Assumptions
 CPU TDP = 135W
 I/O eff = 10pJ/bit 1-side




Future* BW Breakdown

  

2010 estimates based on Intel® Xeon® Processor X7560

*2015-2020 BW need estimates are solely the opinion of the author and do not necessarily represent the position of Intel Corp.

Trends in I/O Power vs. Year*

 

Power efficiency improving

- Driven by circuit, channel and process improvements
- ...but not keeping pace with aggregate BW needs
 - e.g. 1TB/s x 10pJ/bit = 80W!


Impact of 1TB/s CPU*

~1/2 CPU Power Budget

\$800 Electricity


For the environmentally minded:
8000kg of CO²

I/O Energy Efficiency Definition

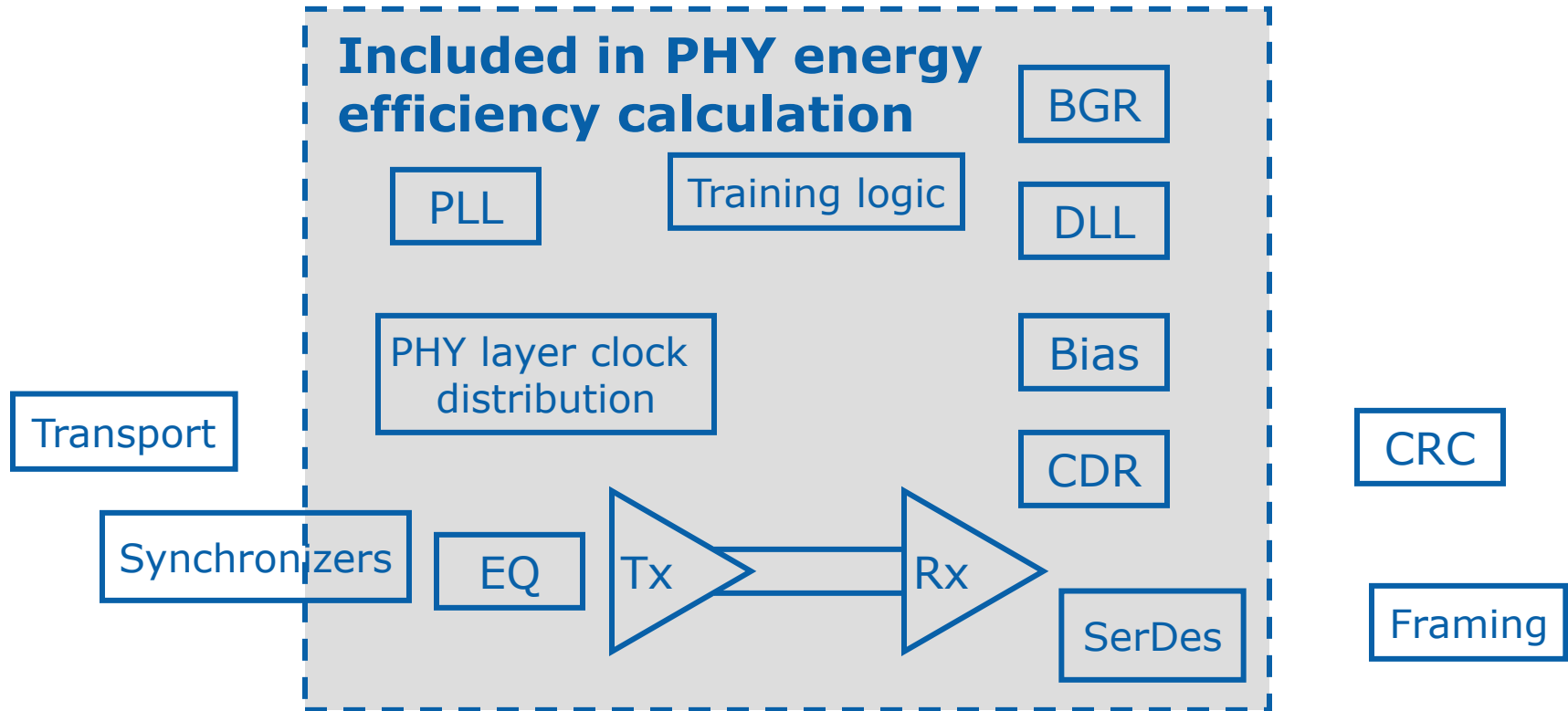


- $\text{mW/Gb/s} = \text{pJ/bit}$
- Total physical layer energy required to move data
 - Includes amortized global power as well
- Usually 2-sided metric (TX + RX)


Agenda

- Introduction
-  Impact of process scaling
- Active power optimization
 - System
 - Circuit
- Power management
- Low power silver bullets
- Putting it all together

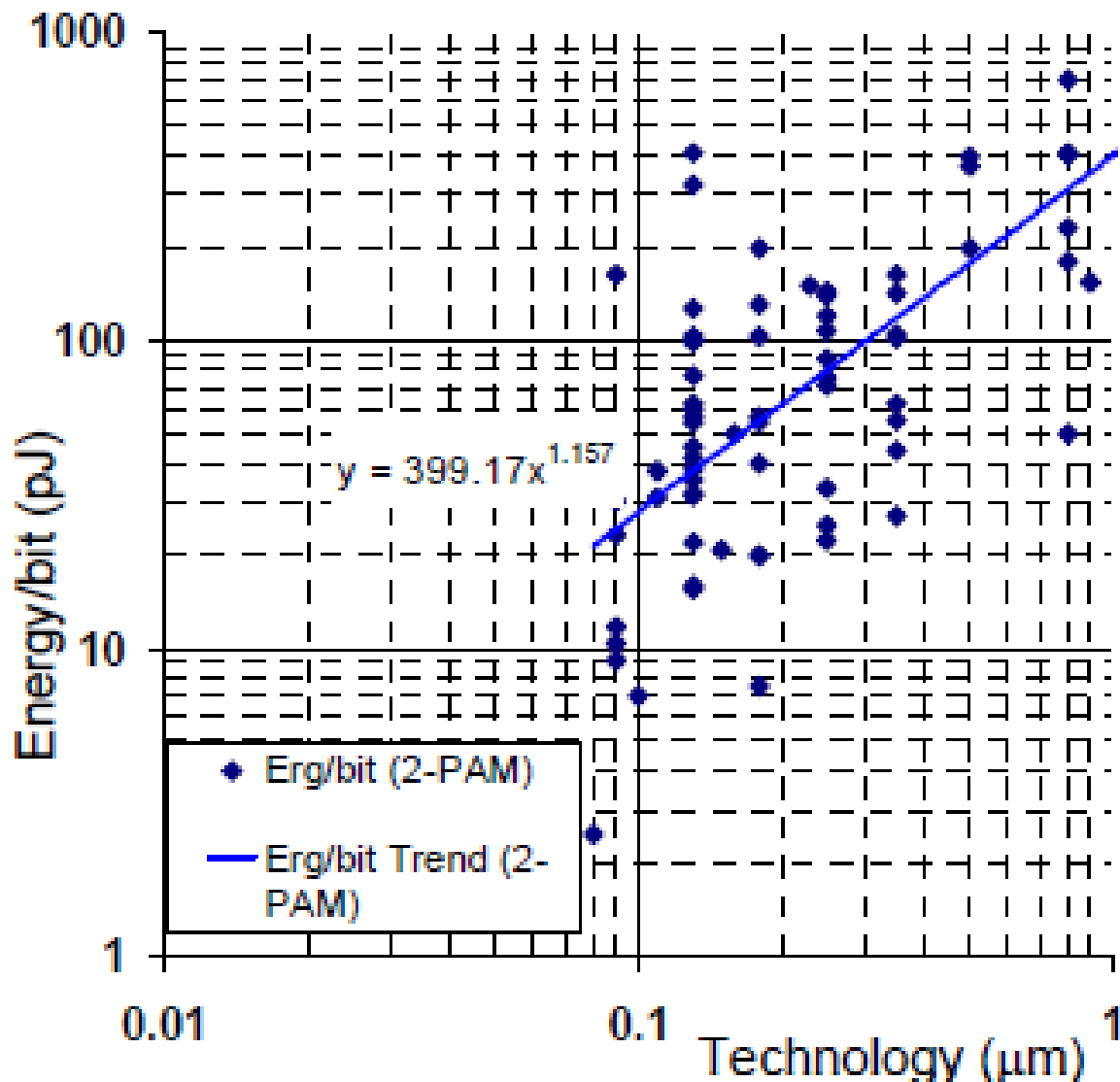Past technology trends scaled efficiency proportional to feature size



Process vs. Logic Scaling Scenarios*

 


*ITRS-like trends assuming bulk planar CMOS. Conceptual scenarios with large error bar.

Example Research I/O Energy Scaling

Process scaling estimates vs. circuit type

- Logic → 0.75x 37
- Noise limited → 0.95x 37.3
- Sense amp → 0.85x 19.2
- Swing limited → 1x 6.5


Research I/O* Power Breakdown

 

**Aggregate I/O
scaling factor
per generation
~0.9x**

**Variation compensation
overhead could cause factor
to be >0.9x**

Trends in I/O Power vs. Year*

 


Architectural enhancements much more effective than process scaling


Agenda

- Introduction
- Impact of process scaling
- Active power optimization
 - ➔ – System
 - Circuit
- Power management
- Low power silver bullets
- Putting it all together


Optimal Energy-Performance Design Space

 


Adder Design Space

 

Adder Design Space

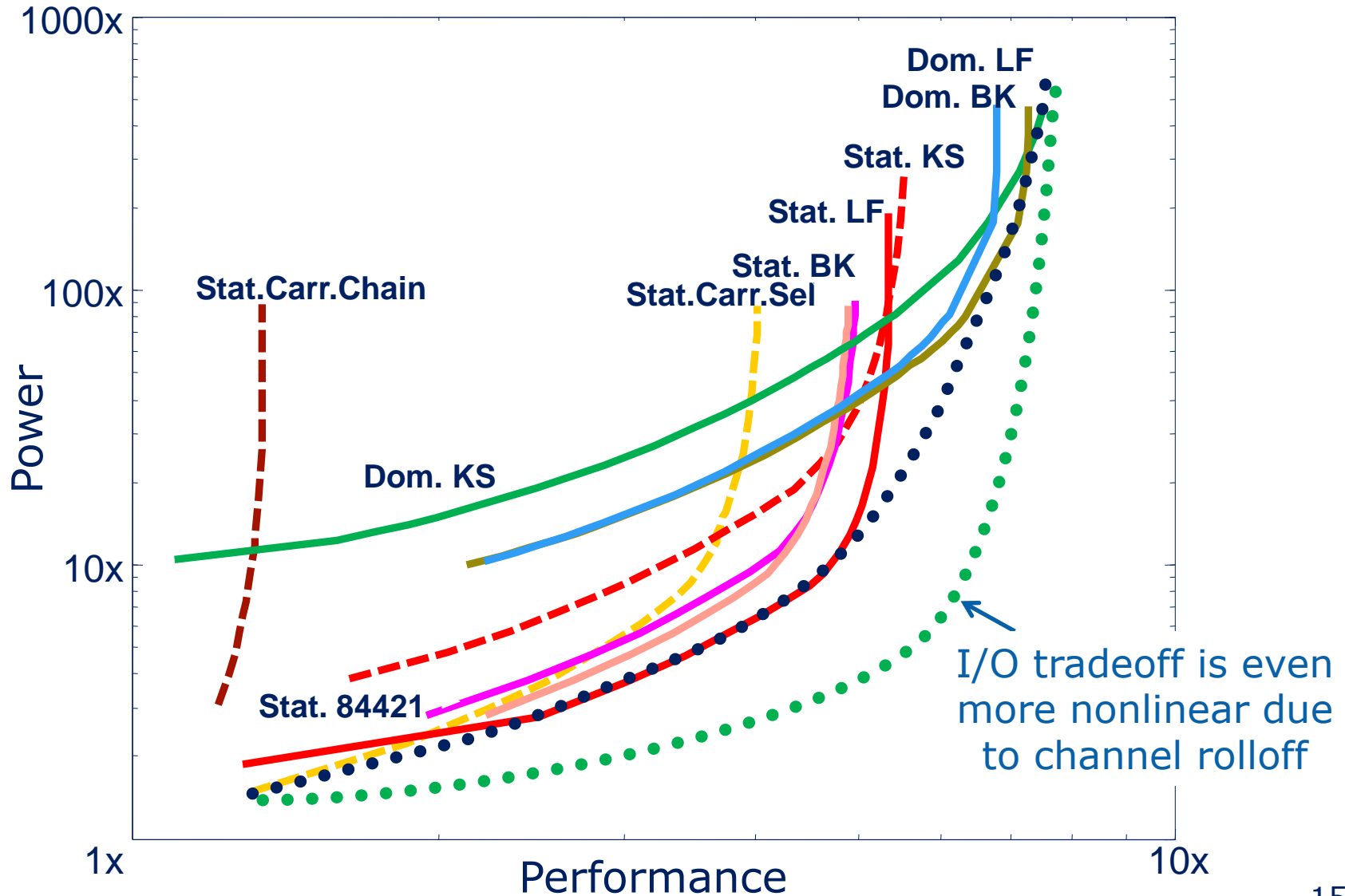

I/O Design Space Tradeoffs

 

Steep tradeoff caused by:

1. Channel BW limit
2. Process BW limit
3. Circuit architecture complexity

Performance

Key to low power links is operating on this portion of design space

Power's Deadly Combination


Stingy System Architect

- Not willing to limit legacy channel length or topologies
- Doesn't want to erode profit margins by adopting higher cost interconnect
- Perceives alternate topologies as unproven & risky
- Annoyed that Moore's law doesn't apply to channels


Macho Link Designer

- Knows Shannon's Capacity
- Takes on challenge to apply advanced communication techniques to high-speed links
 - e.g. DSL, Ethernet
- Thinks Moore's law will eventually resolve power & complexity issues


Energy Efficiency Correlation to Loss

 

Legacy Backplane Channel

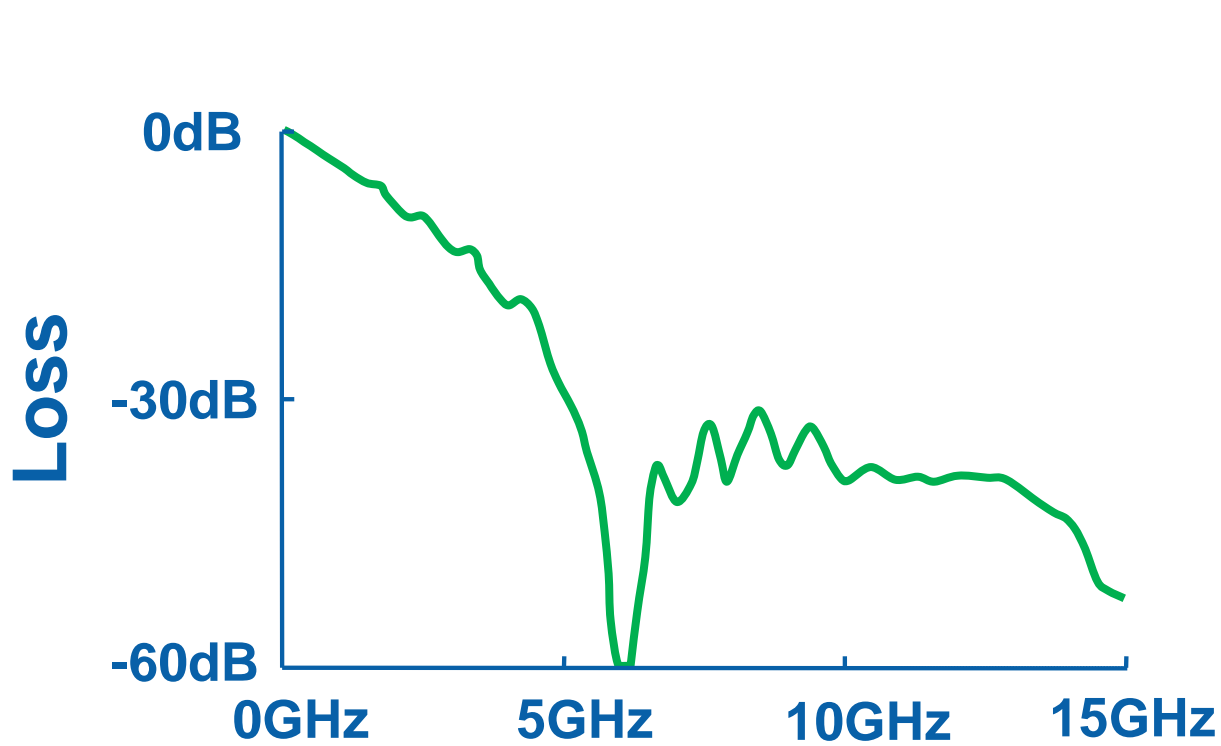


Backplane Data Rates

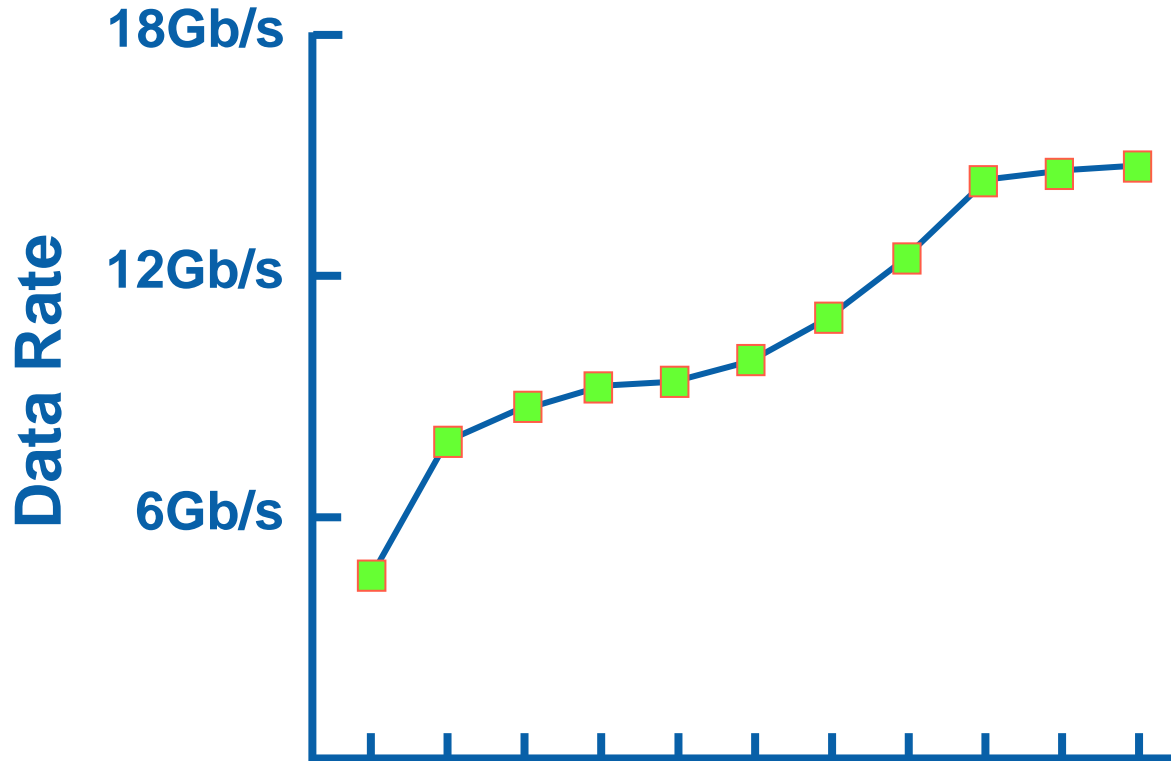

| | | | | | | | | | | | |
|-------------|---|---|---|---|---|---|---|----|----|----|-----|
| TX FIR taps | 1 | 2 | 4 | 4 | 4 | 4 | 4 | 4 | 4 | 4 | 4 |
| DFE taps | | | | 1 | 2 | 4 | 8 | 16 | 32 | 64 | 128 |

→
Increasing Equalizer Complexity (nonlinear scale)


Channel Power Wall

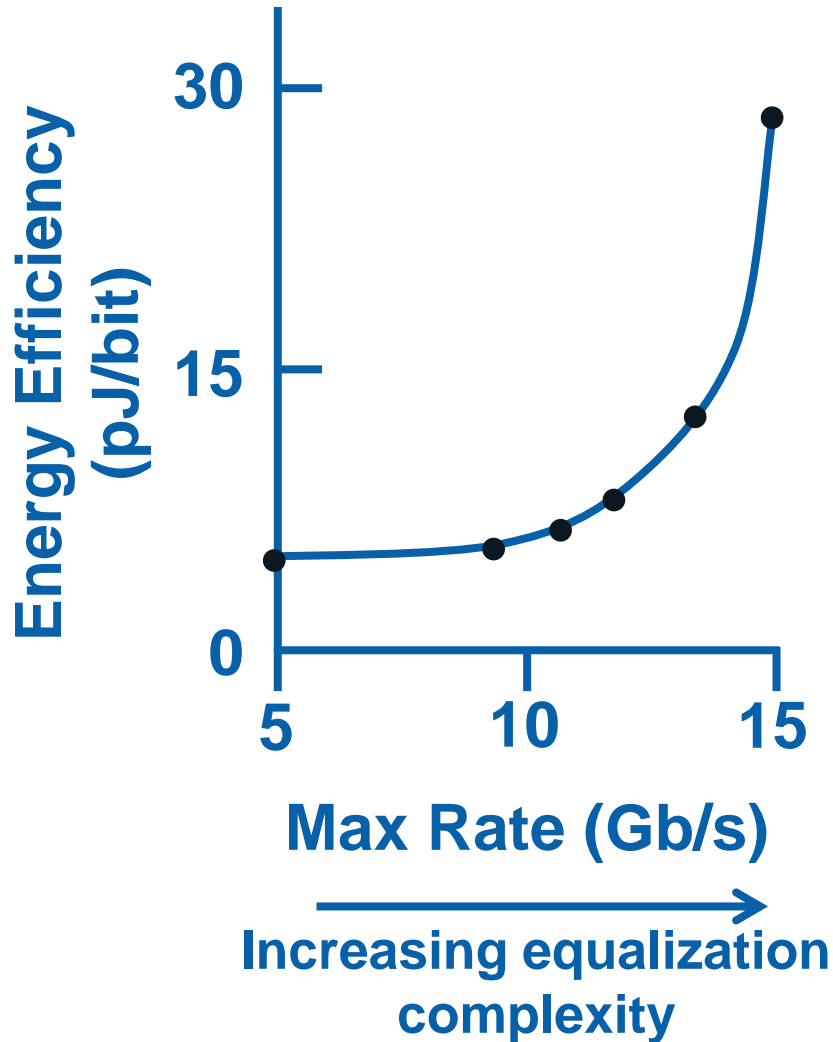


Overextending channel leads to nonlinear EQ power vs. performance tradeoff

I/O Challenges: Power

Insertion Loss

 


 - Legacy backplane w/ 2 connectors & sockets, 1/2m FR4





I/O Challenges: Power


Insertion Loss

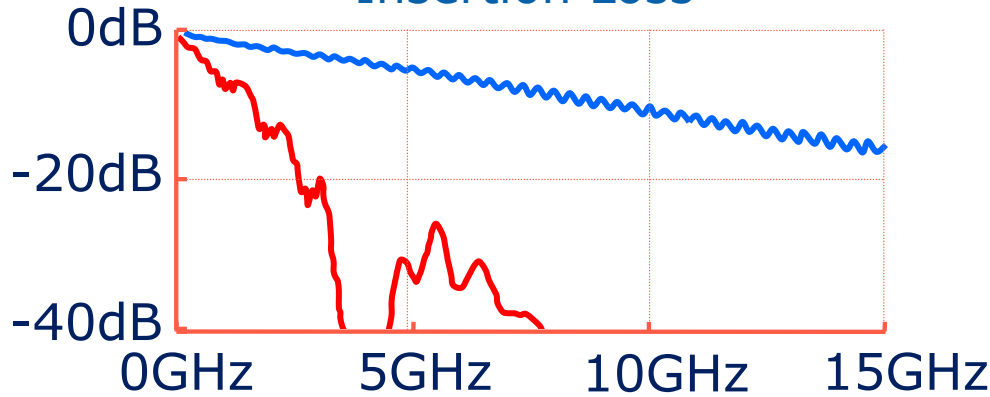

  - Legacy backplane w/ 2 connectors & sockets, 1/2m FR4
- 1/2m cabled topology with top-pkg connectors



Loss/rate/power estimates

 


Assuming:

- Xtalk not primary limiter
- TX+RX jitter $\sim 1/2UI$
- RX noise $1mV_{rms}$
- TX swing $\sim 1V_{diffp-p}$
- Cabled link w/ connectors
– Channel “well behaved”

| Equalization Complexity | Est. data rate | Normalized power (rough guess) |
|--------------------------------|----------------------|--------------------------------|
| None | $\sim 0.8 * X$ Gb/s | 1 |
| Low power | $\sim 2.0 * X$ Gb/s | ~ 1 |
| Moderate (3 tap LE, 4 tap DFE) | $\sim 2.4 * X$ Gb/s | ~ 2 |
| Complex (>50 tap LE+DFE) | $\sim 3.6 * X$ Gb/s | $\sim 10-100$ |
| Complex EQ+PAM+FEC/coding | $\sim 4.4 * X$ Gb/s | $\sim 100-1000$ |
| Shannon's capacity | $\sim 8-10 * X$ Gb/s | n/a |

Common Traits of Low Power Links

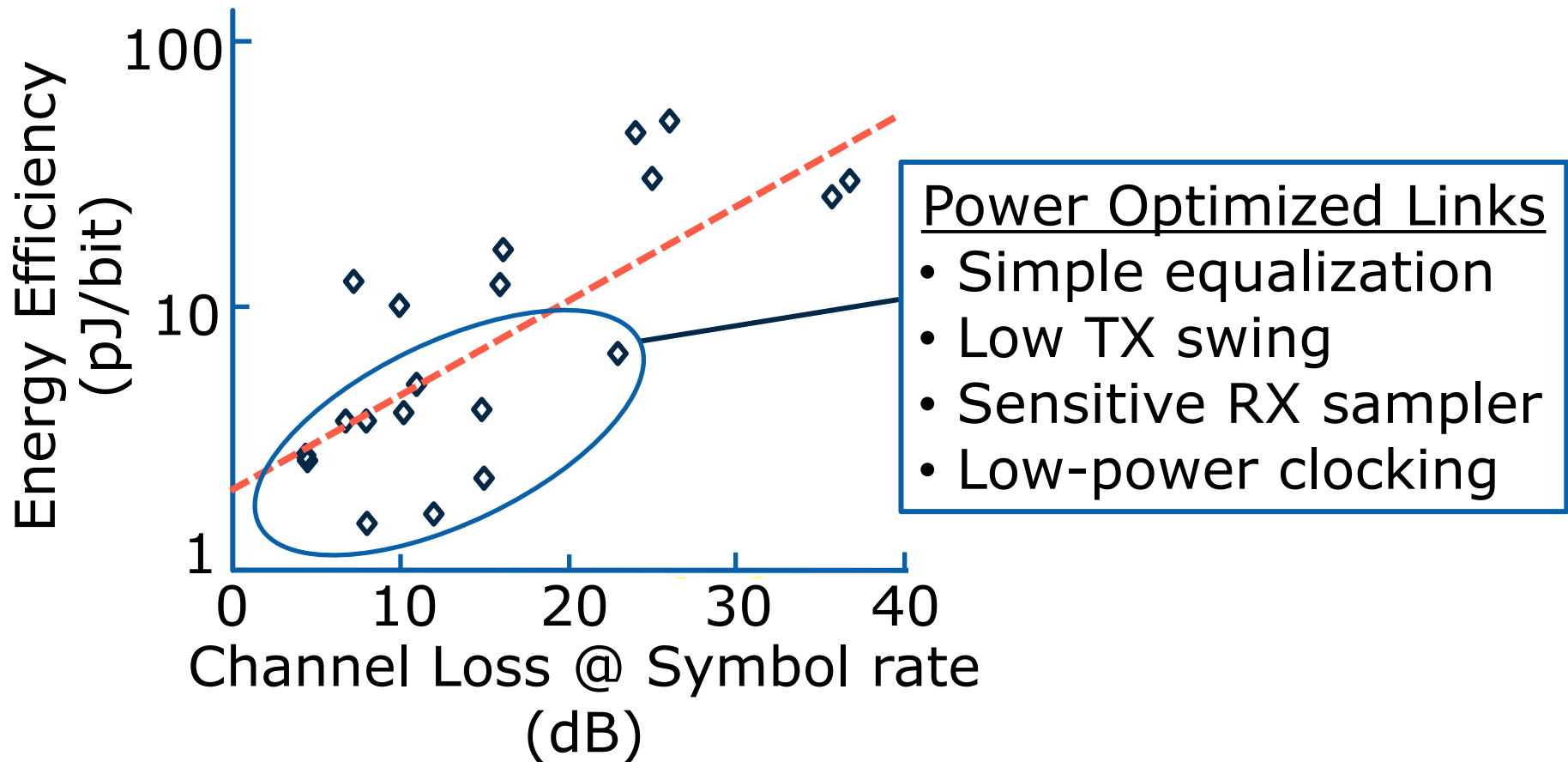


How to scale rate or distance and maintain energy efficiency

- Path to scaling performance: Refined channels
 - e.g. Top-package connector based cabled links


1/2 Meter Channel Examples (based on Intel Labs Measurements)

 - PCIe (2 connector) → 20dB @4GHz
- LCP Flex* → 20dB @15GHz
- Twinax 36 AWG* → 20dB @30GHz



*No connector, pkg or pad cap

Agenda

- Introduction
- Impact of process scaling
- Active power optimization
 - System
 -  – Circuit
- Power management
- Low power silver bullets
- Putting it all together

Low-power Link Circuits Top Ten


- Not a comprehensive list
 - More like a sampling of known power reduction methods
- Few low power links incorporate all of these techniques
 - Most incorporate at least some
- Not intended to be a detailed overview of each method

- 1. Modest data rates**
- 2. Forwarded clocking**
- 3. Global circuit sharing**
- 4. Low power clock distribution**
- 5. Resonantly tuned clocking**
- 6. Low swing TX**
- 7. Sensitive RX**
- 8. Simple equalization**
- 9. Calibration and tuning**
- 10. System modeling**

Top Ten #1: Modest data rates

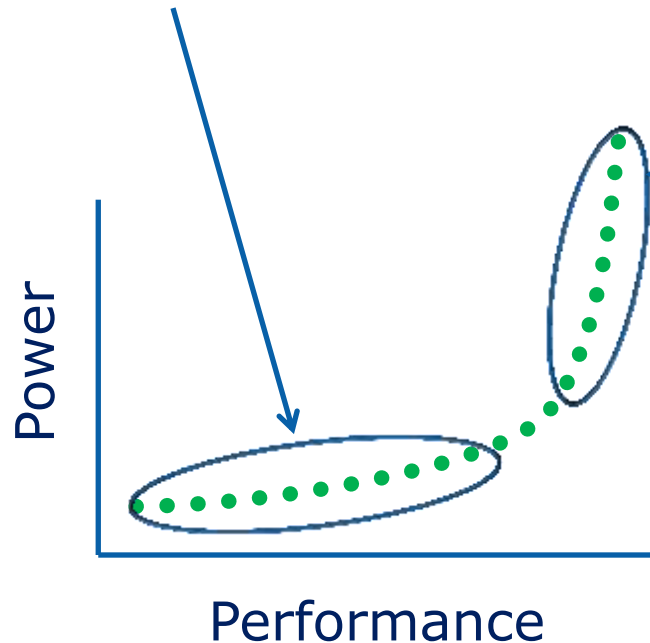1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling


Key to low power links is operating on this portion of design space



Steep tradeoff caused by:

1. Channel BW limit
2. Process BW limit
3. Circuit architecture complexity

Clock Buffer Power/Performance Example

 

Stay off process BW cliff



Performance Impact on Circuit Architecture: Loop-unrolled DFE

Conventional DFE

- Speedpath limits frequency

Loop-unrolled DFE

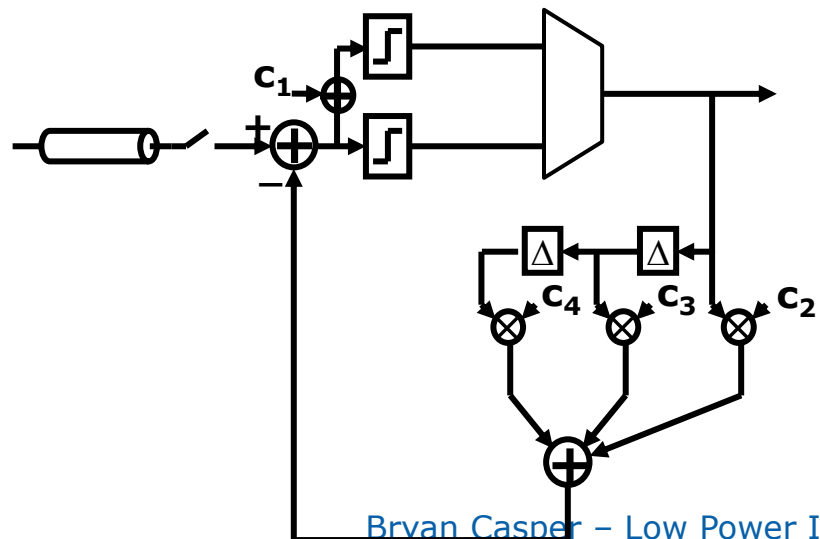 
- Redundancy to alleviate speedpath
- Increases power and complexity
 - Proportional to $C1 \cdot 2^N + C2$
 - $C1$ = comparator + mux
 - $C2$ = baseline power
 - N = number taps unrolled




Performance Impact on Circuit Architecture: Multi-phase Clocking

- Interleaving of receiver alleviates need for high-frequency latches and clocks
- Requires greater clock complexity and calibration
 - Multiphase clock generators
 - Sophisticated phase training


Half rate clock

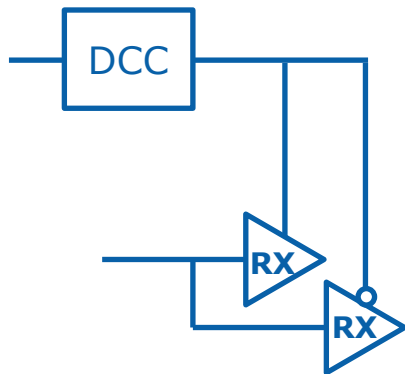


Quarter rate clock

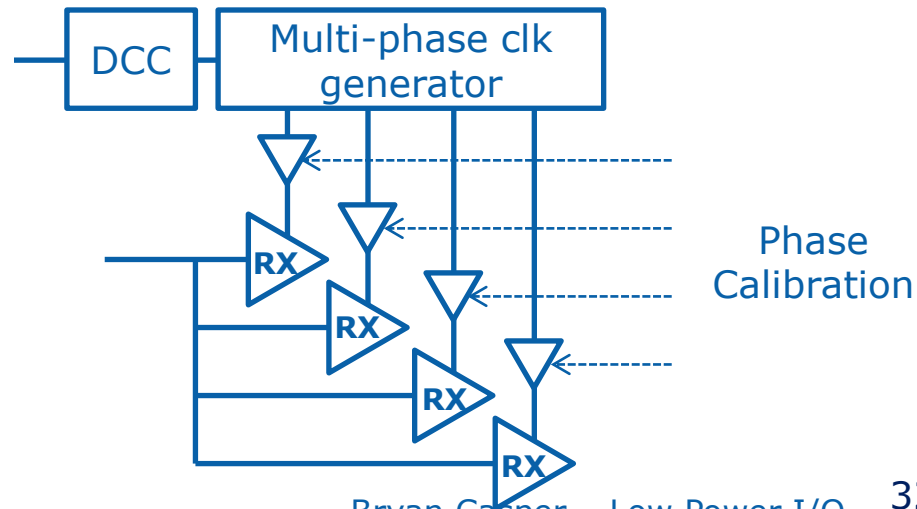

Top Ten #2: Forwarded clocking

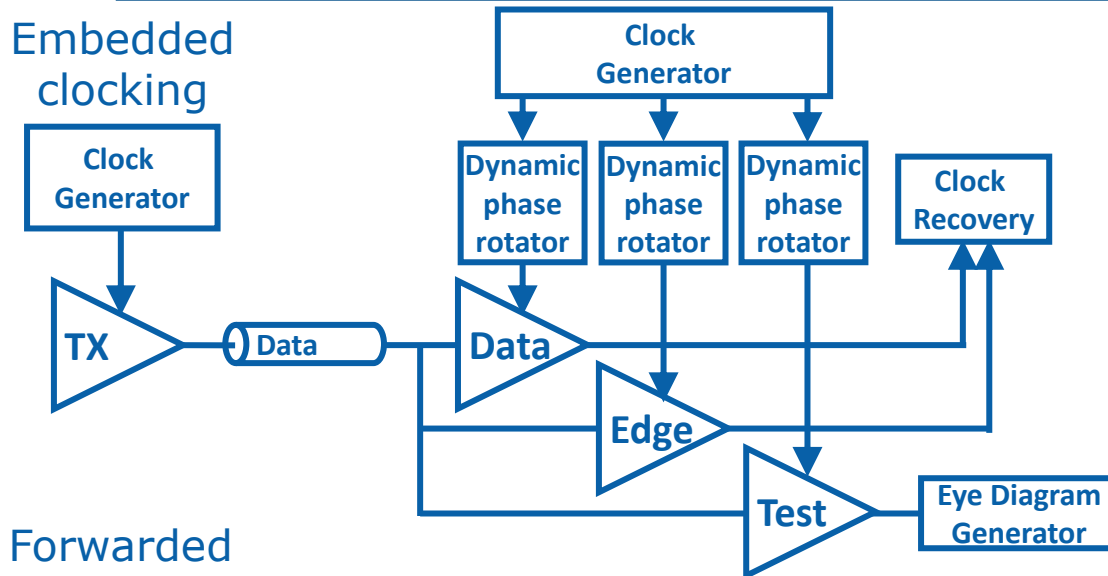

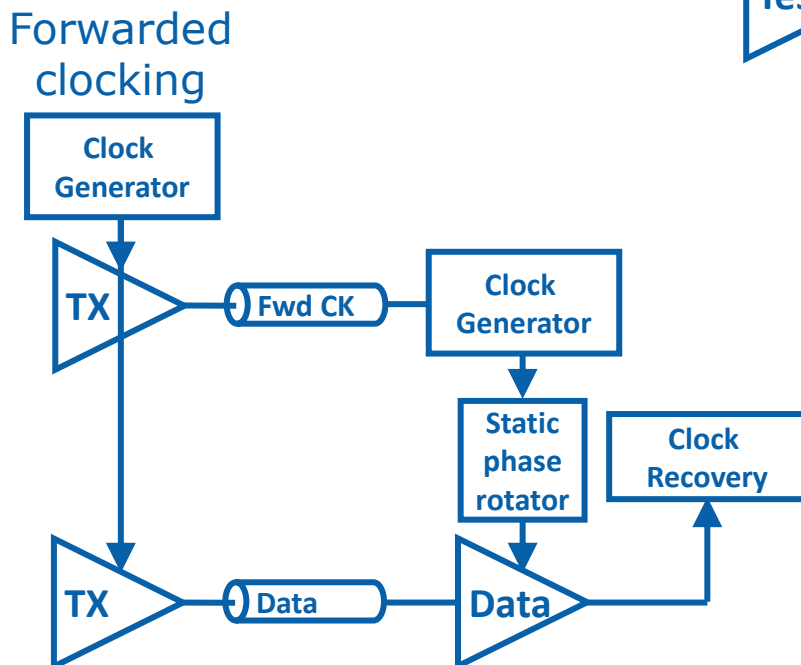1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



Forwarded clock power benefits

- No need for high clock recovery BW
- Edge/test samplers optional
 - Clock recovery/test can be time multiplexed with data samplers
- Fewer, simpler phase rotators
 - Greater tolerance for INL & jitter
 - 1 rotator can cover data, edge & test in a time-multiplexed fashion


Top Ten #3: Global Circuit Sharing

- Parallel link implementations have ample opportunity to share common functionality





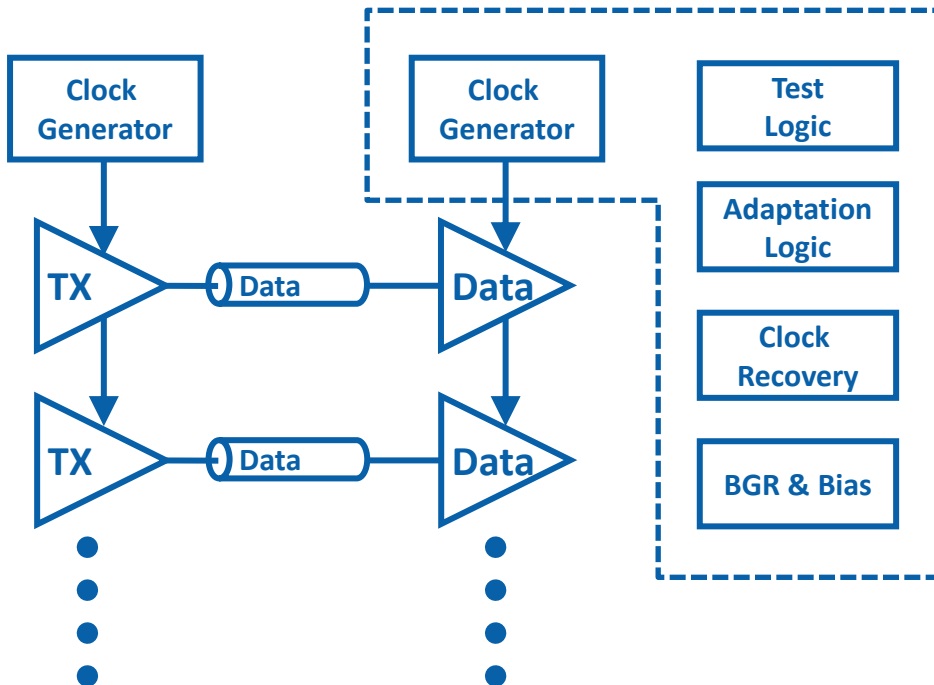1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling

Potential to be shared
across parallel link



  Co-optimization of Channel and Circuits Enables Widespread Power Amortization




- Matched interconnect enables clock recovery sharing
 - Common deskew across 10 bits
- Test, bias, etc. are shared as well

| | | | | | |
|------------|---------------|----------|------|------------|--|
| tx_fclk | Test | Cal. FSM | Bias | Scan | |
| tx_lane[9] | Scan | | | tx_lane[0] | |
| tx_lane[8] | Common deskew | | | tx_lane[1] | |
| tx_lane[7] | | | | tx_lane[2] | |
| tx_lane[6] | | | | tx_lane[3] | |
| tx_lane[5] | Term | | | tx_lane[4] | |

Top Ten #4: Low power clock distribution

- Reduce distribution distance*
 - Compact parallel link floorplan
- Repeaterless distribution**

 
1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. **Low power clock distribution**
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



*F. O'Mahony, et. al., "A 47×10Gb/s 1.4mW/(Gb/s) Parallel Interface in 45nm CMOS," ISSCC 2010

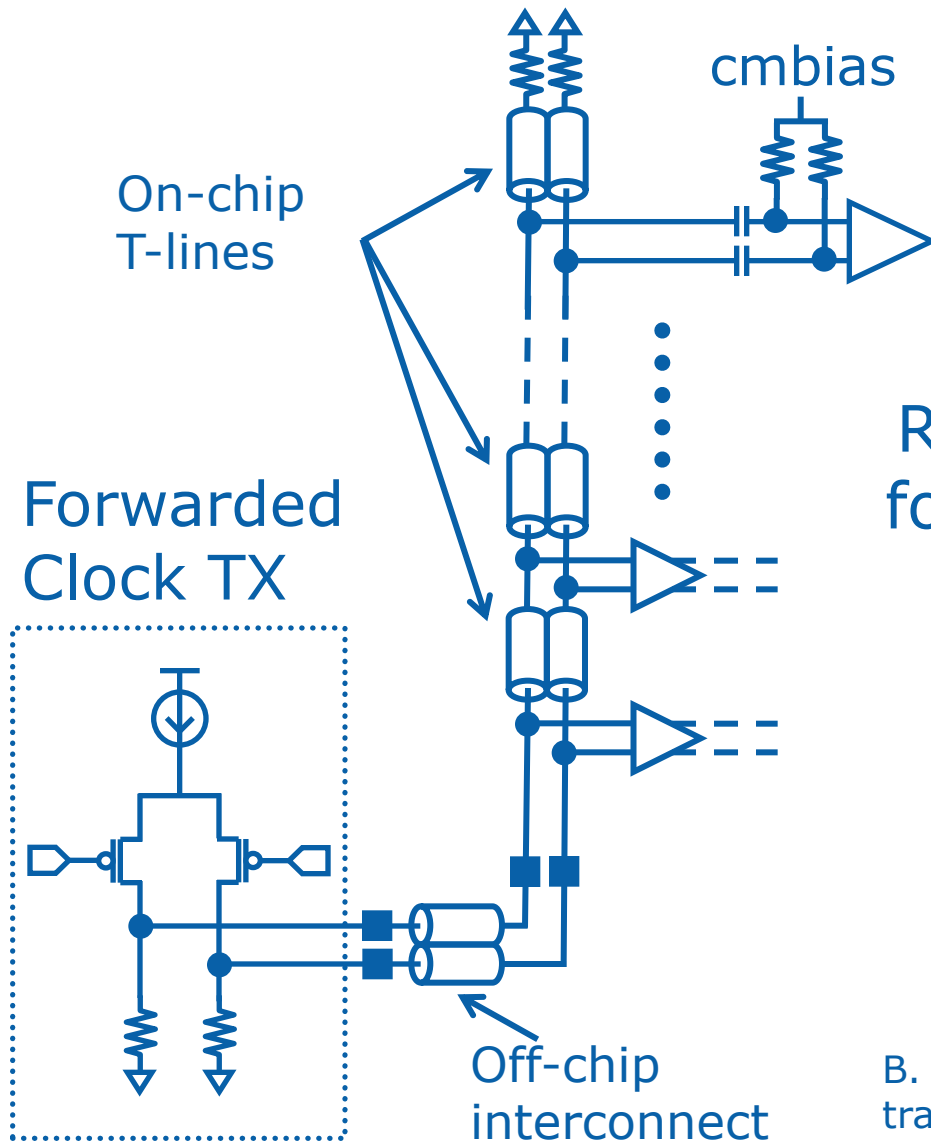**B. Casper, F. O'Mahony, "Clocking Analysis, Implementation and Measurement Techniques for High-Speed Data Links—A Tutorial," TCAS1, Jan. 2009

Forwarded Clock Repeater-less Distribution



Repeater-less distribution +
forwarded clock combination
has potential to eliminate
buffers and save power

B. Casper, et. al., "A 20Gb/s forwarded clock transceiver in 90nm CMOS," ISSCC 2006


Top Ten #5: Resonantly tuned clocking

- Resonant clocking suppresses jitter outside the fundamental clock frequency
- Lower power for a given jitter budget
- Limits clock frequency operating points
- Frequently used for resonators
 - LC-VCO
- Also used for distribution

1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



Resonant Clocking Example

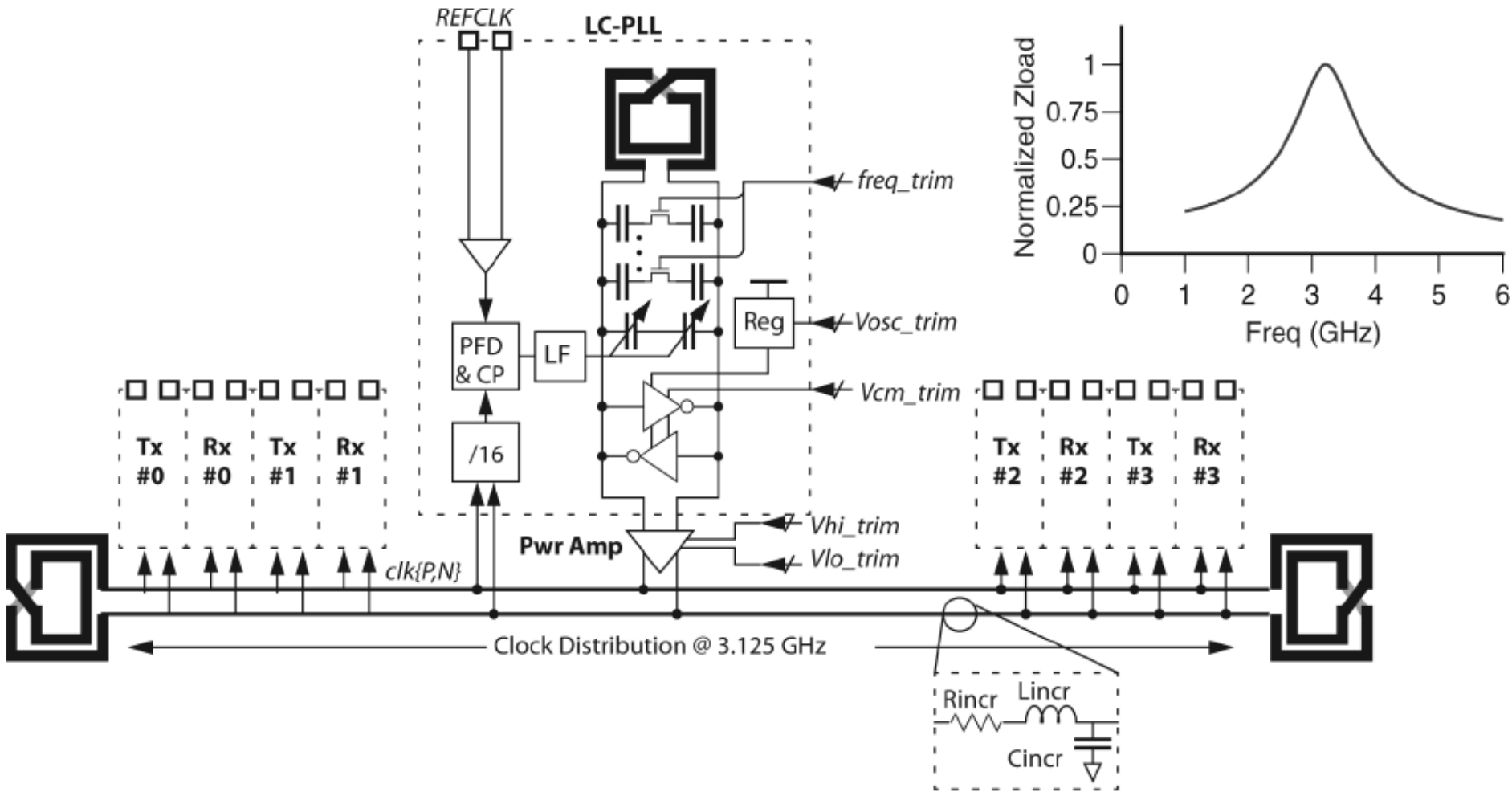

Enabled 3x-5x lower clocking power than conventional distribution


Top Ten #6,7: Co-designed TX & RX

- TX output stage & RX input dissipate a large portion of link power
- Co-optimize to minimize power and meet BER requirements

1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling




Swing vs. RX Sensitivity

 

Assumptions:


- RX noise variance proportional to RX power
 - 5mW \rightarrow 1mVrms
- Normally distributed ISI $\sigma = 0.001 * \text{swing}$
- 1E-12 BER target
- Voltage-mode TX w/ linear reg.
- Channel loss = -20dB

Simplistic Example: Swing vs. Efficiency

 

- Optimal energy at $\sim 160\text{mVpp}$
 - Requires $\sim 1\text{mV}_{\text{rms}}$ input referred RX noise

 Low Swing Tradeoffs: 19" Cabled Link Maximum Rates




- Lowest power equalization points hardly suffer due to low swings.

Top Ten #6: Low-Swing TX

1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



Low-Power TX Drivers: CM vs. VM

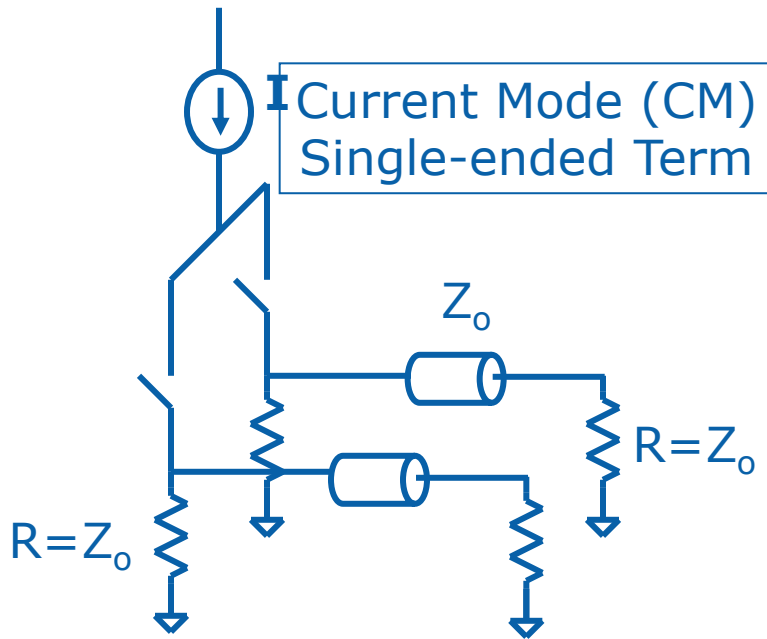

$$V_{d,1} = (I/2)R$$


$$V_{d,0} = -(I/2)R$$

$$V_{d,pp} = IR$$

$$\mathbf{I = (V_{d,pp} / R)}$$

Source: Ganesh Balamurugan

Low-Power TX Drivers: CM vs. VM

 


$$V_{d,1} = (I/2)R$$

$$V_{d,0} = -$$

$$(I/2)R$$

$$V_{d,pp} = IR$$

$$I = (V_{d,pp} / R)$$

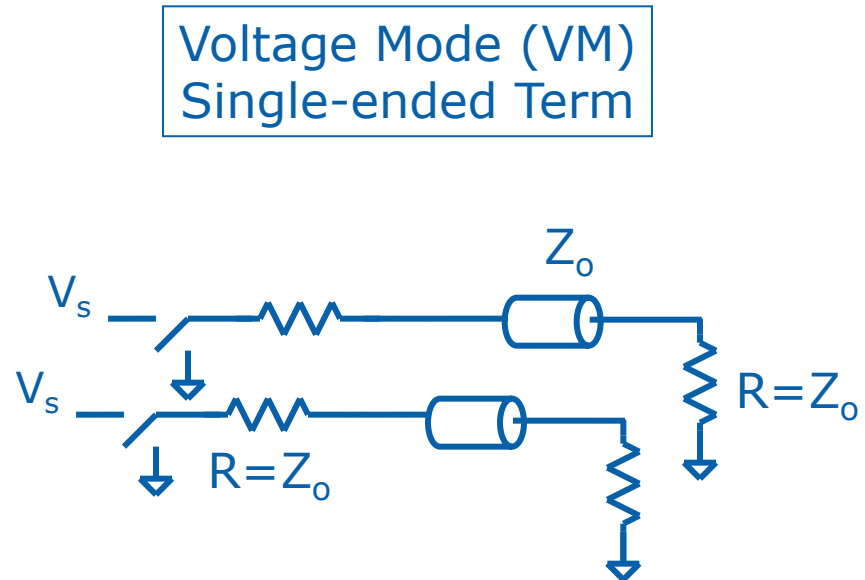

$$V_{d,1} = (V_s / 2)$$

$$V_{d,0} = -(V_s / 2)$$

$$V_{d,pp} = V_s$$


$$I = (V_s / 2R)$$

$$I = (V_{d,pp} / 2R)$$

2X power reduction

Source: Ganesh Balamurugan

Low-Power TX Drivers: CM vs. VM

 


$$V_{d,1} = (I/2)R$$

$$V_{d,0} = -$$

$$(I/2)R = IR$$

$$I = (V_{d,pp} / R)$$

 

$$V_{d,1} = (V_s / 2)$$

$$V_{d,0} = -(V_s / 2)$$

$$V_{d,pp} = V_s$$



$$I = (V_s / 4R)$$

$$I = (V_{d,pp} / 4R)$$

4X power reduction

Source: Ganesh Balamurugan


Low-Swing TX Drivers: CM vs. VM

  


| | VM (Palmer, JSSC 12/2007) | CM (O'Mahony, JSSC 12/2010) |
|---------------------|---------------------------|-----------------------------|
| Vswing | 210mVpp-diff | 150mVpp-diff |
| Proc. / Vcc | 90nm / 1.0Vcc | 45nm / 0.8Vcc |
| Eq. | No | Yes (2-tap) |
| Datarate | 6.25Gb/s | 10Gb/s |
| Bias cap | 36pF | <1pF |
| TX drv power | 1.10mW | 2.12mW |
| TX bias power | 0.76mW | 0.34mW |
| Total TX drv. power | 1.86mW | 2.46mW |

VM power savings reduces for low-swing TX

Top Ten #7: Sensitive RX

1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
-  7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



Low-Power RX samplers

 


Good receiver sensitivity allows low TX swing

- Residual input-referred offset: <2mV
- Input-referred noise: 1mV-rms
- Hysteresis + metastability: <2mV

Sensitive RX samplers

 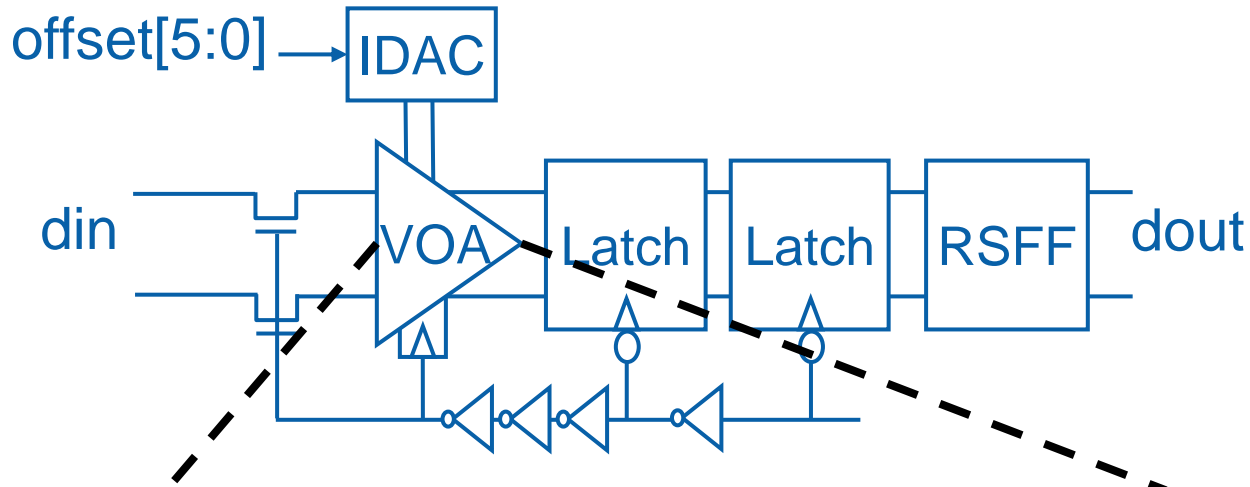


Sensitive RX samplers

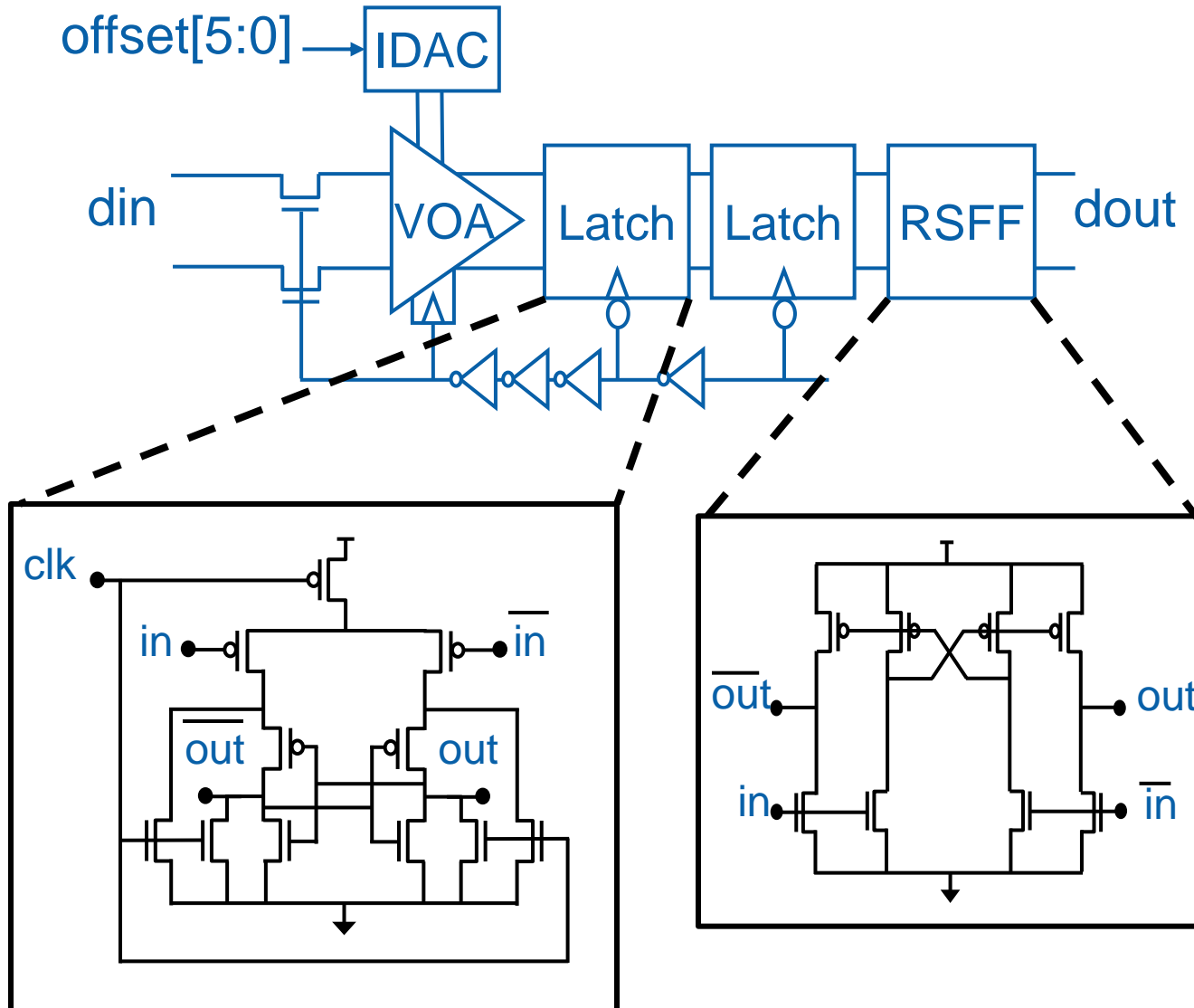

Top Ten #8: Simple Equalization

- Linear equalizers - big bang for the buck
 - If channel is “well behaved” and ISI dominated
- DFE is complex, especially if speedpaths
 - 1-tap DFE only cancels 1 postcursor point

 
1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



 Examples: Low Power Linear Equalizers



- Continuous time linear equalizers

- Passive using HP filters or inductive peaking
- Source degeneration



- Pre-emphasis

  - Limit magnitude & sign of taps
- Current summing in analog domain




Top Ten #9: Calibration and tuning

- Process scaling may reduce power
 - By scaling both C and V scaling
 - Increases variation due to smaller device area
- Increased logic resources enables sophisticated calibration logic to compensate variation

 1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling




$$\sigma V_T = \frac{1}{\sqrt{2}} \left(\frac{C_2}{\sqrt{W_{\text{eff}} \cdot L_{\text{eff}}}} \right)$$



K. Kuhn, IEDM 2007

Extrapolated Process Variation

 


| | | |
|--------------|---------|---------|
| ◆ C2_hi | 5.9E-09 | 5.6E-09 |
| ■ C2_lo | 5.9E-09 | 4.9E-09 |
| ▲ std(Vt_hi) | 1.4E-02 | 2.6E-02 |
| ■ std(Vt_lo) | 1.4E-02 | 2.3E-02 |

Area & Energy scaling
limited by variation

$$\sigma(V_t) = C2 \div \sqrt{A_{\text{gate}}}$$

Example: Phase Rotator


Adapted/Calibrated

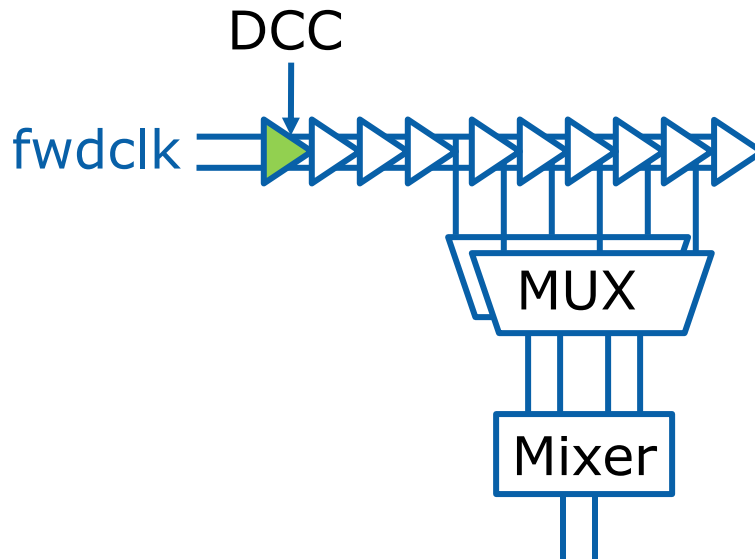

Most calibration and adaptation used today is fairly basic

- e.g. duty cycle correction

Example: Programmable Phase Rotator

 

- Power can scale as process variation increases
- Alternative is to not scale device area and hence no power scaling

Top Ten #10: System Modeling

- Key to low power is balanced implementation
 - Achieved through comprehensive understanding of power/performance tradeoffs
- Focus design effort and power on highest impact components
- System-level optimization most impactful
 - Most will not have this opportunity due to standardization specs.
 - Sub-system optimization still useful


1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling



Methodology example: Sensitivity Calculation to Optimize Power

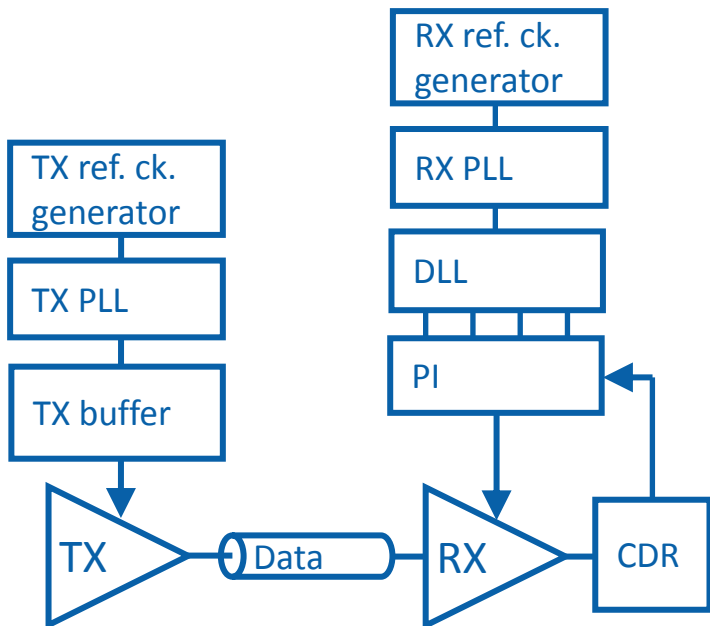1. Calculate 1st order power sensitivity of each design option
2. Calculate 1st order margin sensitivity of each design option
3. Form mathematical relationship between power and performance
4. Minimize power for performance target using optimization algorithm
5. Repeat steps 1-4 to further refine design point

Methodology example: Sensitivity Calculation to Optimize Power



| Parameter change | Baseline change | Eye width change estimate vs. baseline (units = 1ps or 0.01UI) | Power delta estimate vs. baseline (mW) |
|---|-----------------|--|--|
| Baseline eye width | | 18 | 100 |
| TX ref. ck. jitter (pp) | 50ps→60ps | -4 | +0 |
| TX PLL 1-UI jitter , rms (Gaussian jitter, accumulated) | 0.5ps→0.75ps | -12 | -3 |
| TX equalizer | 2 taps → 3 taps | -2 | +3 |
| TX swing | 100mV → 200mV | +3 | +4 |
| TX buffer sinusoidal jitter @ 200MHz | ±15ps→±18ps | -10 | -1 |
| TX buffer duty cycle error | 1% →2% | -1 | -0.1 |
| RX PLL 1-UI jitter , rms (Gaussian jitter, accumulated) | 0.5ps→0.75ps | +0 | -3 |
| RX PLL bandwidth | 4MHz→6MHz | -7 | +0 |
| CDR loop latency | 2UI→4UI | -2 | -1 |
| RX input noise | 1mVrms→2mVrms | -2 | +2 |
| PI phase accuracy | 0.015UI→0.03UI | -1 | -3 |

Knowledge of system performance and power sensitivities enables global power optimization

Agenda

- Introduction
- Impact of process scaling
- Active power optimization
 - System
 - Circuit

Power management

- Low power silver bullets
- Putting it all together

Server Utilization



 


Figure 1. Average CPU utilization of more than 5,000 servers during a six-month period.


Energy-Disproportionate Link

 

Energy-proportional I/O

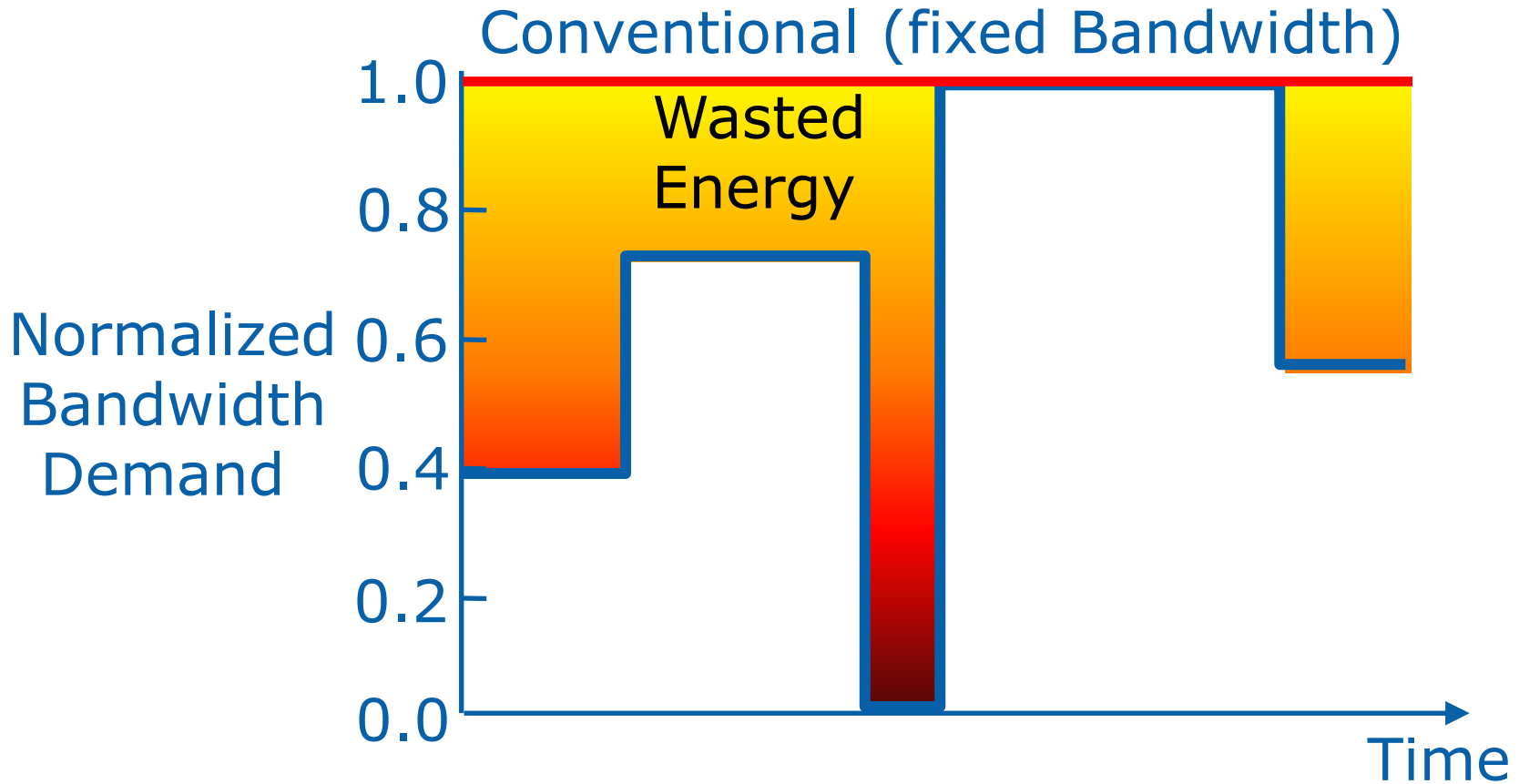


Power Management: Scalable supplies

 


Power efficiency improves with adaptive supply/biasing

Refs: B. Casper, ISSCC '06 & G. Balamurugan, JSSC 4/08


65nm Low Power Link Operating Points

 

 Benefit of Eliminating Excess BW: Non-linear Efficiency/Performance



Fast Wake-Up Clcking

 


O'Mahony et al, "A 47x10Gb/s 1.4mW/(Gb/s) Parallel Interface in 45nm CMOS," ISSCC, Feb. 2010.

Agenda

- Introduction
- Impact of process scaling
- Active power optimization
 - System
 - Circuit
- Power management
- ➔ Low power silver bullets (?)
- Putting it all together


Low Power Link “Silver Bullets”?

Optical

 


Modulation (PAM)

3D Stacking

 

Silver Bullet?: Optical

 
- Claim:
 - Optical power is inherently better because no equalization needed
- Reality:
 - Most optical power claims only include optical components
 - Disregards electrical driver, clocking, recovery, synchron., serdes, etc.
 - Optical link = Electrical link + optical components in the middle
 - Optical/electrical power crossover is likely 1m-5m, depending on rate




Stay on this portion of the curve and equalization power likely to be small subset of overall link power (e.g. <5% [O'Mahony,ISSCC2010])

Apples-Apples Electrical/Optical Channel Comparison


- Electrical

 


- Optical

 

Complete Optical CPU Link

 

 Example Optical Loss Profile (consumer electronics)




- Optical channel loss is frequency independent
 - But the aggregate loss is 100x-1000x!
- VCSEL or MZI based links require large swings (500mV-1V)
- Worst-case received signal can be as low as ~10uA
 - Requires extremely sensitive receiver (costs power)
- Full optical link >2x power of electrical at $\leq 3\text{m}$ distance

Silver Bullet?: PAM


- Claim:
 - PAM uses less BW resulting in less equalization and lower power
- Reality:
 - No inherent performance/power advantage over binary
 - Using practical channels and $1E-12$ BER
 - Equalization and clock recovery more difficult
 - PAM receiver more complex
 - 4 PAM requires 1.5 samples/bit + decoding
 - Binary requires 1 sample/bit
 - PAM may have advantages when
 - Symbol rate limited due to circuits
 - Channel has excess BW

 Max data rate with 1e-12 BER (LE & DFE 4-tap)



RS(64,48,8) Coding overhead estimated at 100pJ/bit in 65nm

 Max data rate with small block coding to achieve $1e-12$ BER (LE & DFE 4-tap)



RS(64,48,8) Coding overhead estimated at 100pJ/bit in 65nm


45nm PAM Measurements (Within-package channel)

| Channel | Signaling Mode | Efficiency | Data rate | TX swing |
|------------|----------------|------------|-----------|----------|
| MCP | 2-PAM | 2.3pJ/bit | 12.5G | 120mV |
| | 3-PAM | 2.6pJ/bit | 18.75G | 260mV |
| | 4-PAM | 2.6pJ/bit | 25G | 360mV |

- Modulation benefits links that have channel BW much greater than circuit BW
- For this example, 2PAM power expected to be higher than 4PAM (at same data rate)
 - Due to circuit limitations

Silver Bullet?: 3D Stacking

 
- Claim:
 - Stacking minimizes need for high-speed I/O
- Reality:
 - Potential to reduce I/O power (within stack) by 10x-100x
 - Reduce C & V (CV^2)
 - Components within stack must be tightly integrated (architecture, process, mechanicals)
 - Thermal and power delivery limits applicability
 - Primarily applicable for low power stacks



Micron Hybrid Memory Cube

 Example: Stacking DRAM on CPU

- Multiple DRAM stacks on CPU constrain power due to thermals
 - DRAM temp limit $<100^{\circ}\text{C}$
 - Assumes standard CPU cooling solution



- **Primarily applicable for low power CPUs**
- **Micro-channel cooling could change tradeoffs**

Low Power Link “Silver Bullets”?


Optical

Modulation (PAM)


3D Stacking

Each technology may have power advantages for a limited set of applications. However, not a general solution to solving the Link Power Problem.



Agenda

- Introduction
- Impact of process scaling
- Active power optimization
 - System
 - Circuit
- Power management
- Low power silver bullets
-  Putting it all together


Example: 47x10Gb/s Interface

 

Solutions: Interconnect

  

Solutions: Connectors

 

Top-pkg connector
(4 signals/mm²)


Solution: Circuits

- Utilized most suggested low power optimizations


1. Modest data rates
2. Forwarded clocking
3. Global circuit sharing
4. Low power clock distribution
5. Resonantly tuned clocking
6. Low swing TX
7. Sensitive RX
8. Simple equalization
9. Calibration and tuning
10. System modeling

Low Power Prototype Results

0.5m flex interconnect

 


3m twinax cable

 

45nm CMOS prototype demonstrates industry leading I/O power efficiency with non-traditional interconnects

Low Power Prototype Results


Link data rate = 10Gb/s

 

Aggressive power management:

- Idle mode is 93% less power than active state
- Wake-up from idle <5ns

Research Roadmap

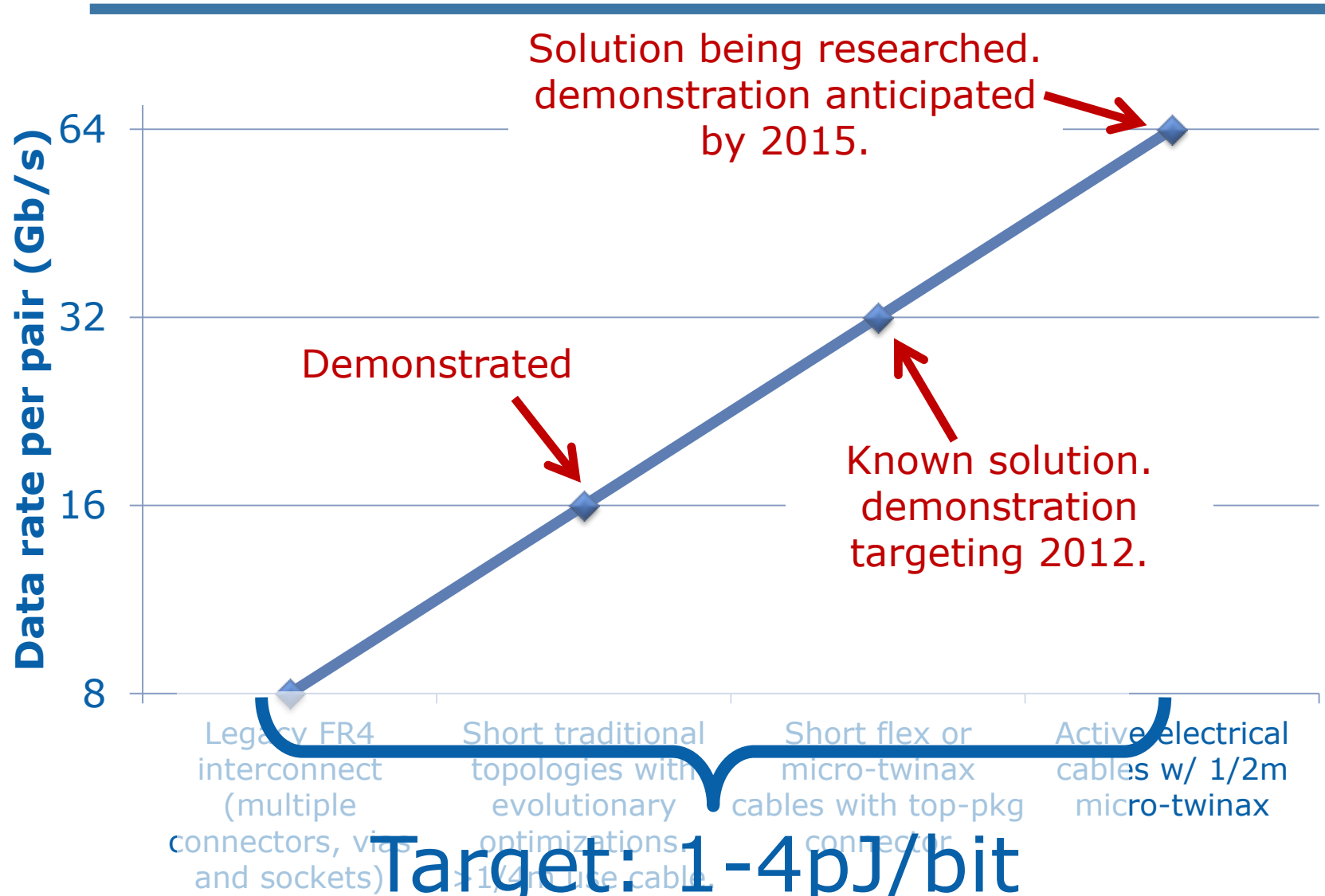

Target: 1-4pJ/bit
(vs. current product=20-40pJ/bit)

Link Active Power Optimization Key Points

- 1TB/s socket BW needed by 2020
 - Power optimize or I/O will require majority of power budget
- Don't depend solely on process scaling to lower power
 - Architecture and circuit will drive energy scaling
- Stay away from bleeding edge
 - Channel, process and architecture
- Balanced link design is key to low power
- Optical & stacking promising but limited
- Electrical innovation in circuits and channel fruitful

Acknowledgement: Frank O'Mahony, James Jaussi, Ganesh Balamurugan, Mozghan Mansuri, Sudip Shekhar

Related Publications 1

- F. O'Mahony, et al., "A 47×10 Gb/s 1.4mW/(Gb/s) parallel interface in 45nm CMOS," *IEEE Int. Solid-State Circuits Conf. Dig. Tech. Papers*, Feb. 2010, pp. 156–157.
- F. O'Mahony, et al., "The future of electrical I/O for microprocessors," *International Symposium on VLSI DAT*, Apr. 2009, pp. 31-34.
- G. Balamurugan, et al., "A scalable 5–15Gbps, 14–75mW low-power I/O transceiver in 65 nm CMOS," *IEEE J. Solid-State Circuits*, vol. 43, pp. 1010-1019, Apr. 2008
- H. Braunisch, et al., "High-speed flex circuit chip-to-chip interconnects," *IEEE Trans. On Advanced Packaging*, vol. 31, no. 1, 2008, pp. 82-90.
- B. Casper, et al., "Future microprocessor interfaces: analysis, design and optimization," *IEEE Custom Integrated Circuits Conference*, Sept. 2007, pp. 479 – 486.

Related Publications 2

- J. Poulton, R. Palmer, A. M. Fuller, T. Greer, J. Eyles, W. J. Dally, and M. Horowitz, "A 14-mW 6.25-Gb/s transceiver in 90-nm CMOS," *IEEE J. Solid-State Circuits*, vol. 42, pp. 2745-2757, Dec. 2007.
- H. Hatamkhani, F. Lambrecht, V. Stojanovic, and C.-K. K. Yang, "Power-centric design of high-speed I/Os," in *Proc. Design Automation Conf.*, 2006, pp. 867-872.
- K.-L. J. Wong, H. Hatamkhani, M. Mansuri, and C.-K. K. Yang, "A 27-mW 3.6-Gb/s I/O transceiver", *IEEE J. Solid-State Circuits*, vol. 39, pp. 602-612, Dec. 2004.
- G. Balamurugan, J. Kennedy, G. Banerjee, J. E. Jaussi, M. Mansuri, F. O'Mahony, B. Casper, and R. Mooney, "A scalable 5–15 Gbps, 14–75 mW low-power I/O transceiver in 65 nm CMOS," *IEEE J. Solid-State Circuits*, vol. 43, pp. 1010-1019, Apr. 2008.
- S. Joshi, J. T.-S. Liao, Y. Fan, S. Hyvonen, M. Nagarajan, J. Rizk, H.-J. Lee, and I. Young, "A 12-Gb/s transceiver in 32-nm bulk CMOS," in *2009 Symp. VLSI Circuits Dig. Tech. Papers*, pp. 52-53.
- B. Leibowitz, R. Palmer, J. Poulton, Y. Frans, S. Li, J. Wilson, M. Bucher, A. M. Fuller, J. Eyles, M. Aleksić, T. Greer, and N. M. Nguyen, "A 4.3 GB/s mobile memory interface with power-efficient bandwidth scaling," *IEEE J. Solid-State Circuits*, vol. 45, pp. 889-898, Apr. 2010.
- F. O'Mahony, M. Mansuri, B. Casper, J. E. Jaussi, and R. Mooney, "A low-jitter PLL and repeaterless clock distribution network for a 20Gb/s link", in *2006 Symp. VLSI Circuits Dig. Tech. Papers*, pp. 36-37.
- B. Casper, J. E. Jaussi, F. O'Mahony, M. Mansuri, K. Canagasaby, J. Kennedy, E. Yeung, and R. Mooney, "A 20Gb/s forwarded clock transceiver in 90nm CMOS," in *2006 IEEE ISSCC Dig. Tech. Papers*, pp. 90-91.
- J. Montanaro, R. T. Witek, K. Anne, A. J. Black,, E. M. Cooper, D. W. Dobberpuhl, P. H. Donahue, J. Eno, G. W. Hoepfner, D. Kruckemyer, T. H. Lee, P. C. M. Lin, L. Madden, D. Murray, M. H. Pearce, S. Santhanam, K. J. Snyder, R. Stephany, and S. C. Thierauf, "A 160-MHz, 32-b, 0.5-W CMOS RISC microprocessor," *IEEE J. Solid-State Circuits*, vol. 31, pp. 1703–1714, Nov. 1996.

Related Publications 3

- Intel® Core™ i5-670 Processor <http://ark.intel.com/Product.aspx?id=43556>
- Intel® Xeon® Processor X5670 <http://ark.intel.com/Product.aspx?id=47920>
- Intel® Xeon® Processor X7560 <http://ark.intel.com/Product.aspx?id=46499>
- O'Mahony, F.; Kennedy, J.; Jaussi, J.E.; Balamurugan, G.; Mansuri, M.; Roberts, C.; Shekhar, S.; Mooney, R.; Casper, B.; , "A 47×10Gb/s 1.4mW/(Gb/s) parallel interface in 45nm CMOS," *Solid-State Circuits Conference Digest of Technical Papers (ISSCC), 2010 IEEE International* , vol., no., pp.156-157, 7-11 Feb. 2010
- Horowitz, M.; Alon, E.; Patil, D.; Naffziger, S.; Rajesh Kumar; Bernstein, K.; , "Scaling, power, and the future of CMOS," *Electron Devices Meeting, 2005. IEDM Technical Digest. IEEE International* , vol., no., pp.7 pp.-15, 5-5 Dec. 2005
- Casper, B.; Balamurugan, G.; Jaussi, J.E.; Kennedy, J.; Mansuri, M.; , "Future Microprocessor Interfaces: Analysis, Design and Optimization," *Custom Integrated Circuits Conference, 2007. CICC '07. IEEE* , vol., no., pp.479-486, 16-19 Sept. 2007
- B. Casper, F. O'Mahony, "Clocking Analysis, Implementation and Measurement Techniques for High-Speed Data Links—A Tutorial," *TCAS1*, Jan. 2009
- Casper, B.; Jaussi, J.; O'Mahony, F.; Mansuri, M.; Canagasaby, K.; Kennedy, J.; Yeung, E.; Mooney, R.; , "A 20Gb/s Forwarded Clock Transceiver in 90nm CMOS B.," *Solid-State Circuits Conference, 2006. ISSCC 2006. Digest of Technical Papers. IEEE International* , vol., no., pp. 263- 272, Feb. 6-9, 2006
- Kuhn, K.J.; , "Reducing Variation in Advanced Logic Technologies: Approaches to Process and Design for Manufacturability of Nanoscale CMOS," *Electron Devices Meeting, 2007. IEDM 2007. IEEE International* , vol., no., pp.471-474, 10-12 Dec. 2007
- F. O'Mahony, B. Casper, M. Mansuri, M. Hossain, "A Programmable Phase Rotator Based on Time-Modulated Injection-Locking," *VLSI symposium* 2010